



B.Tech II Year I Semester Supplementary Examinations, February 2021  
Network Analysis

(Electronics and Communication Engineering)

Maximum Marks: 70

Date: 01.03.2021 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 The resistance of two wires is  $30 \Omega$  when connected in series and  $6 \Omega$  when connected in parallel. Determine the resistance of each wire.
- 2 A series RC circuit has  $R = 5 \Omega$  and  $C = 10 \mu\text{F}$ . Find time constant.
- 3 Define transient time.
- 4 How the damping ratio defines various types of damping?
- 5 What is excitation and response?
- 6 Write the expressions for root mean square and average value of a periodic waveforms.
- 7 What is iterative impedance?
- 8 Why Transfer functions are used in the analysis of the networks?
- 9 What is composite image filters?
- 10 Define Foster's reactance theorem.

Part-B

Answer All the following questions.

(10M X 5=50Marks)


- 11 i) Define the following terms

(4M)

a. Branch b. Sub Graph c. Noded. Tree

- ii) For the graph given below find incidence and cut-set matrices

(6M)

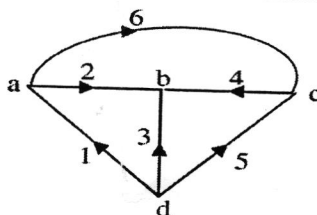


OR

- 12 Derive the Mutual inductance and the coupling coefficient of the transformer with necessary illustrations.

- 13 Derive the expression for voltage  $V(t)$  in source free RC circuit. (10M)

OR

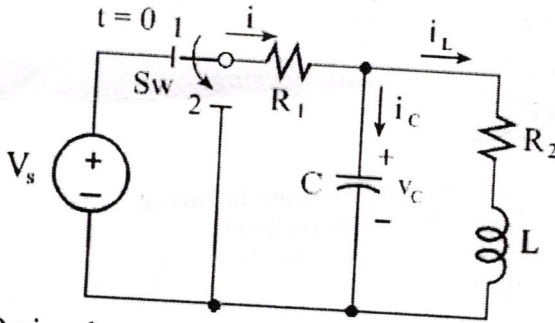- 14 In the following RLC circuit if  $R_1 = 2 \Omega$ ,  $R_2 = 10 \Omega$ ,  $L = 0.1H$ ,  $C = 0.8mF$  and  $V_s = 120V$ , then find out the transient response of the inductive current after the switch is thrown from position 1 to 2 at  $t = 0$ . (10M)



- 15 Derive the expression for current  $I(t)$  in source free RL circuit. (10M)

OR

- 16 A series RLC circuit has  $R = 4 \Omega$ ,  $C = \frac{1}{2} F$ ,  $L = 2H$  and connected with DC source of  $v = \frac{1}{2} e^{-4t}$ . Determine the voltage  $v_o$  across the impedance in the circuit. Assume zero initial conditions. (10M)

- 17 The Z parameters of a two-port network are  $Z_{11} = 10 \Omega$ ,  $Z_{22} = 15 \Omega$ ,  $Z_{12} = Z_{21} = 5 \Omega$ . Find the equivalent T network and ABCD parameters. (10M)

OR

- 18 Explain about symmetry and reciprocity in Z parameters. (10M)

- 19 i) Design a symmetrical lattice attenuator to have characteristic impedance of  $800 \Omega$  and attenuation of 20 dB. (5M)  
 ii) Design a symmetrical bridged T- attenuator with an attenuation of 20 dB and terminated into a load of  $500 \Omega$ . (5M)

OR

- 20 Explain about LPF and HPF in detail. (10M)