



R18 Regulation

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY  
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 2P3BC

B.Tech III Semester Regular/Supplementary Examinations, February 2021

**ELECTRONIC CIRCUITS**  
(Electrical and Electronics Engineering)

Maximum Marks: 70

Date: 22.02.2021 Duration: 3 hours

- Note: 1. This question paper contains two parts A and B.  
2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.  
3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.  
4. Each question carries 10 marks and may have a, b, c, d as sub questions.

## Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Define amplifier? List the types of amplifiers?
- 2 What is Miller effect?
- 3 Classify negative feedback amplifiers.
- 4 Write the conditions for Oscillations and its sustenance.
- 5 Mention the achievable Maximum efficiency of Class -A amplifiers.
- 6 Discuss the importance of heat sinks.
- 7 What is high pass circuit?
- 8 Distinguish between comparators and clipping circuits.
- 9 Explain how does diode acts as a switch?
- 10 List the applications of Schmitt trigger?

## Part-B

Answer All the following questions.

(10MX 5=50Marks)

- 11 A. Draw the CC amplifier and derive the expression for  $A_i$ ,  $R_i$ ,  $A_v$ ,  $Y_o$ . (5M)  
B. A CE amplifier is drawn by a voltage source of internal resistance  $R_S = 800$  ohms and load impedance is a resistance  $R_L = 1000$  ohms. The h-parameters are  $h_{ie} = 1.0K$  ohms,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 50$  and  $h_{oe} = 25 \mu A/V$ . compute  $A_i$ ,  $R_i$ ,  $A_v$  and  $R_o$  using exact analysis. (5M)
- OR
- 12 A. Mention the significance of Gain Bandwidth product of amplifiers. (5M)  
B. Draw and explain the effect of coupling and bypass capacitors on low-frequency response of CE Amplifier. (5M)
  - 13 Determine the effect of negative feedback on the input and output impedances of a Voltage-Series feedback amplifier. Show the circuit schematic diagram. (10M)
- OR
- 14 Discuss the operation of Wein-Bridge oscillator with necessary diagrams. (10M)
  - 15 A. Discuss the operation of Transformer coupled Class- A amplifiers with diagram. (5M)  
B. What are the draw backs of transformer coupled power amplifier. (5M)

