



B.Tech II Year II Semester Supplementary Examinations, July 2021
PULSE AND DIGITAL CIRCUITS
(ECE)

Maximum Marks: 70

Date: 19.07.2021 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks **(10x2M=20 Marks)**

- 1 Obtain the response of high pass RC circuit for a ramp input.
- 2 Define % tilt of RC circuit.
- 3 Write down the applications of clipping Circuit?
- 4 Draw Negative biased Negative clipper circuit.
- 5 Draw the piecewise linear diode characteristics.
- 6 When transistor acts as a switch?
- 7 Define multivibrator.
- 8 What is purpose of collector catching diodes?
- 9 What is difference between sampling gate and logic gate?
- 10 Define fan-out.


Part-B

Answer All the following questions. **(10MX 5=50Marks)**

- 11 Draw the output of the low pass RC circuit for different time constant to: a) Pulse input b) Step input. [10M]

OR

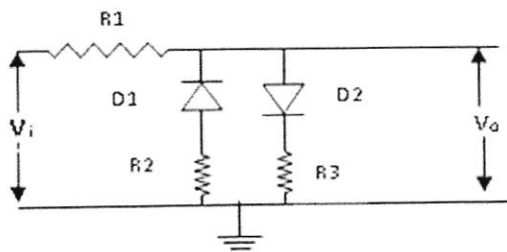- 12 Derive the expression for percentage tilt for a square wave output of RC high pass circuit. [10M]
- 13 a) Explain the operation of diode comparator. Briefly mention various applications of comparators. [5M]
b) Diodes are ideal diodes write transfer equation and draw the transfer characteristics. if $V_i = 40 \sin \omega t$ indicate all voltage levels. ($R_1 = R_2 = R_3 = 1k\Omega$) [5M]



OR

- 14 a) List out the few differences between clipper and clamper with examples. [5M]
b) Define Clamping Circuit Theorem and explain its operation when the capacitor value is very large. [5M]
- 15 a) Demonstrate with neat diagrams the behavior of the diode as switch and define various switching times. [5M]
b) Draw the switch circuit using transistor and find the collector to emitter voltage when input is 0V and +5V(V_{CC}) [5M]
- OR
- 16 Draw the circuit diagram of the relaxation oscillator using UJT and derive the expression for frequency of oscillations. [10M]
- 17 a) Draw the circuit diagram of Emitter-coupled monostable multivibrator and explain its operation in detail. [5M]
b) What is hysteresis and explain the different methods for avoiding hysteresis in Schmitt trigger in detail. [5M]
- OR
- 18 Draw and explain the working principle of astable multivibrator circuit and also explain the merits and limitations of it. And also derive the expression for its pulse width. [10M]
- 19 Discuss in detail the sine wave frequency division with a sweep circuit. [10M]
- OR
- 20 Draw and explain 2-input NAND gate with functional table. [10M]