



Regulation R17

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY  
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 1P6BB

**B.Tech III Year II Semester Supplementary Examinations, June 2022**  
**POWER ELECTRONICS**

(EEE)

Maximum Marks: 70

Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 What losses occur in a thyristor during working conditions.
- 2 What are the factors that affect the turn off time of SCRs?
- 3 What is commutation angle or overlap angle?
- 4 What is meant by input power factor in controlled rectifier?
- 5 What are the two types of cyclo-converters?
- 6 What is an AC voltage controller?
- 7 What is meant by voltage commutation?
- 8 What is meant by frequency modulation control in a dc chopper?
- 9 Why thyristors are preferred for inverter circuit
- 10 What are the main classifications of inverter

Part-B

Answer All the following questions.

(5X10M=50Marks)

- 11 a) Explain the construction of SCR with neat diagram. Draw its V-I characteristics. 7  
b) What are the applications of power MOSFET? 3
- 12 Explain the operation of IGBT with VI and switching characteristics. 10
- 13 A single-phase semi converter delivers to RLE load with  $R=5\Omega$ ,  $L=10\text{mH}$  and  $E=80\text{V}$ . The source voltage is 230V, 50Hz. For continuous conduction, Find the average value of output current for firing angle  $\alpha=50^\circ$ . 10
- 14 Discuss the operation of single-phase semi converter and derive the output voltage expression. 10
- 15 a) Explain the operation of single-phase step-up cycloconverter with RL load. 5  
b) A single-phase half wave AC voltage controller, using one SCR in antiparallel with a diode. Feeds 1kW, 230V heater. Find the load power for a firing angle of (i)  $0^\circ$  (ii)  $180^\circ$  (iii)  $70^\circ$ . 5

OR

- 16 a) Distinguish between an ac voltage controller and a cyclo-converter with respect to operation and control aspects. 5  
b) Derive an expression for rms value of output voltage of single-phase ac voltage controller. 5
- 17 Explain working principle of AC chopper with necessary diagrams 10

OR

- 18 a) Derive expressions for minimum and maximum values of load current in a step down chopper with R-L-E load. 5  
b) A step-up chopper has a source of 250 V (dc) in series with inductance of 0.1 H. If the semiconductor switch is operated with different values of duty ratio, plot output voltage vs duty ratio 5
- 19 A 3-phase bridge inverter is operated in  $180^\circ$  conduction mode. Derive output line voltage and phase voltage expression. 10

OR

- 20 A six-step three-phase inverter has an adjustable dc input. The load is a balanced Y connection with a series RL combination in each phase, with  $R = 5 \Omega$  and  $L = 50 \text{ mH}$ . The output frequency is to be varied between 30 and 60 Hz. Determine the range of the dc input voltage required to maintain the fundamental-frequency component of current at 10 A (rms). 10