



R18 Regulation *Subject code: 2E8BF*
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
(Autonomous, Accredited by NAAC with 'A' Grade)

B.Tech VIII Semester Regular/Supplementary Examinations, April 2023

Electrical Drives

(Electrical and Electronics Engineering)

Maximum Marks: 70

Date: 05.05.2023 Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Write the expression for average output voltage of full converter fed separately excited dc drive.
- 2 Differentiate between semi converters and fully controlled converters
- 3 Mark the four quadrant operations of the drive on speed-torque plane.
- 4 If a dual converter is used as a drive, how do you set the firing angles to operate in the third quadrant?
- 5 What are the different types of control schemes of Dc choppers.
- 6 Mention the range of duty cycle for choppers.
- 7 Define slip speed control.
- 8 What are the types of slip power recovery system.
- 9 What are the factors effecting speed of synchronous motor.
- 10 Write torque equation of synchronous motor

Part-B

Answer All the following questions.

(5X10M=50Marks)

- 11 A. A 220V, 1200 RPM, 80A separately excited DC motor has armature resistance 0.2Ω , which is fed from a single-phase full converter with ac input 230V, 50Hz for continuous conduction. Determine: [5]
 - (a) Firing angle and rated motor torque at 700rpm.
 - (b) Motor speed for $\alpha=150^\circ$ and half rated torque.
- B. Explain speed-torque characteristic and voltage versus firing angle curves at different firing angles for a single-phase semi converter fed with a separately excited DC motor. [5]

OR

- 12 Single-phase fully controlled thyristor converter is supplying a separately excited DC Motor. Draw the relevant waveforms and explain various operating modes of the drive. [10]
- 13 Explain Multi quadrant operation of a DC drive consider the example as A Hoist. [10]

OR

- 14 A. Explain the operation of the single phase dual converter and draw the characteristics. [5]
B. Analyze the closed-loop control of a DC drive using suitable block diagram. [5]
- 15 A 230V, 960 rpm and 200A separately excited DC motor has an armature resistance of 0.02Ω . The motor is fed from a chopper which provides both motoring and braking operations. Assuming continuous conduction. Calculate: [10]
(a) Duty ratio for motoring operation at rated torque and 350rpm.
(b) Duty ratio for braking operation at rated torque and 350rpm
- OR
- 16 A. Explain the operation of chopper fed separately excited DC motor. [5]
B. Explain four applications of Closed-Loop Control of DC Drive. [5]
- 17 A. Draw and explain speed control of 3-phase induction motor using AC voltage controller. [5]
B. At 50 Hz the synchronous speed and full load speed are 1500 rpm and 370 rpm respectively. Calculate the approximate value speed for a frequency of 30 Hz and 80% of full load torque for inverter fed induction motor drive. [5]
- OR
- 18 A. A 400V, 50Hz, 3-phase squirrel cage induction motor develops full load torque at 1470 rpm. If supply voltage reduces to 340 V, with load torque remaining constant, calculate the motor speed. Assume speed-torque characteristics of the motor to be linear in the stable region. Neglect stator resistance. [5]
B. Explain the principle of operation static Kramer drive method with suitable circuit diagrams and characteristics. [5]
- 19 A. Draw and explain speed-torque characteristics of VSI fed self-controlled synchronous motor drive. [5]
B. Compare self-controlled and separate controlled mode of operation of synchronous motor drive. [5]
- OR
- 20 A. Discuss why frequency control of induction motor is more efficient than stator voltage Control. [5]
B. Distinguish between Synchronous motor drive and Induction motor drive. [5]