



B.TECH I SEMESTER SUPPLEMENTARY EXAMINATIONS, APRIL 2022

BASIC ELECTRICAL ENGINEERING
(Common to CE,EEE,ME &IT)

Max. Marks: 70

Date: 07.05.2022 Duration: 3 hrs

NOTE: This question paper contains two parts A&B. Part A is compulsory which carries 20 marks. Answer all questions in part A. Part B consists of 5 units. Answer any one full question from each unit Each question carries 10 marks and may have a,b,c

Part-A

Answer all the following

10X2M=20M

- 1 Define Ohms law & mention its Limitations.
- 2 Discuss Faradays law of electromagnetic induction.
- 3 Change the following rectangular quantities into polar.
a) $15+j40$ (b) $10-j20$
- 4 Define the terms i)Time Period and ii)Average Value
- 5 Define Norton's theorem and draw the Norton's equivalent circuit.
- 6 State the Tellgen's theorem.
- 7 Define the EMF.
- 8 Compare ideal transformer and practical transformer.
- 9 Mention the importance of Earthing.
- 10 List the types of Cables.

Part-B

Answer All the following questions.

Marks: 5X10M =50M

- 11 Explain KCL & KVL with an example

10M

OR

- 12 Build the expression for self-inductance, mutual inductance and coefficient of coupling of magnetic circuit.

10M

- 13 Derive the expression for Form factor and Peak factor value of sinusoidal waveform.


10M

OR

- 14 Estimate the Voltage, current and power equations and draw the phasor diagram of RL parallel ac circuit

10M

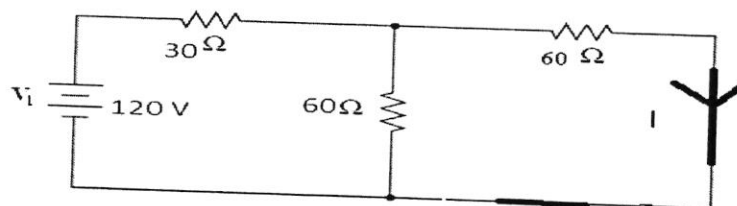- 15 Find current through 60 Ohm resistor for the following circuit using Norton's Theorem. 10M



OR

- 16 Explain maximum power transfer theorem with suitable example (AC) and derive the expression for maximum power delivered to the load. 10M
- 17 Explain the following terms in a DC machine with neat diagram 10M
- i. Yoke
 - ii. Armature core
 - iii. Armature winding
 - iv. Commutator
 - v. Brushes
- OR
- 18 Explain the operation of a single phase transformer under 10M
- i) Lagging load
 - ii) Leading load
- with neat diagrams
- 19 (i) Compare meter board and distribution board 5M
(ii) Explain about Battery backup. 5M
- OR
- 20 Explain characteristics of Batteries. 10M