



B.Tech I Semester Supplementary Examinations, April 2022
ELECTRONIC DEVICES AND CIRCUITS

(Common to ECE & CSE)

Maximum Marks: 70

Date:07.05.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Define space charge region in a PN junction Diode
- 2 Define cutin volage of PN junction diode.
- 3 Draw the symbol and V-I characteristics of SCR diode.
- 4 Write the applications of Varactor Diode
- 5 Write the difference between HWR and FWR.
- 6 Draw the circuit diagram of Bridge Rectifier using pi filter.
- 7 Define Early effect.
- 8 Explain Thermal runaway
- 9 Write the differences between BJT and FET.
- 10 Draw the symbols of JFET and MOSFET?

Part-B

Answer All the following questions.

(5X10M=50Marks)

- 11 Draw and explain forward and reverse bias characteristics of P-N junction diode with neat sketches. [10]

OR

- 12 a. Explain Diode Resistance and derive Dynamic resistance. [5]
b. Determine the value of forward current for a pn junction with $I_o = 15 \mu A$, $V_f = 0,6V$, at $T=300K$. Assume silicon diode. [5]
- 13 Explain the operation of a Tunnel Diode using Energy band diagrams. [10]

OR

- 14 Explain the V-I characteristics of Zenar diode and its applications. [10]
- 15 Draw the circuit and explain the operation of a Bridge Rectifier. [10]

OR

- 16 Draw and explain the circuit diagram of full wave rectifier with L-section filter. [10]

17 Explain the input and output characteristics of CE configured transistor circuit with a neat circuit diagram. [10]

OR

18 a. Define α β and γ . Write relation between α β and γ

b. Determine the operating point for a fixed bias circuit whose $V_{cc}=12V$, $R_c=4K\Omega$, $R_b=930K\Omega$, $\beta=50$ for a silicon transistor. [5+5]

19 Explain Drain & transfer characteristics of JFET and give the advantages of JFET. [10]

OR

20 Explain the construction and operation of a Enhancement MOSFET and draw its characteristics. [10]