



R20 Regulation

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code:3E1AD

B.Tech I Semester Regular/Supplementary Examinations, April 2022

BASIC ELECTRICAL ENGINEERING

(Common to CE &EEE)

Maximum Marks: 70

Date: 07.05.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)


- 1 State Kirchhoff's laws.
- 2 State maximum power transfer theorem.
- 3 Define Form-factor.
- 4 Draw the Phasor diagram for a series RL circuit.
- 5 How to reduce the eddy current losses in transformer.
- 6 Define efficiency in transformer.
- 7 Write EMF equation of DC generator.
- 8 What is back EMF?
- 9 What is the need of earthing?
- 10 What are methods available to improve power factor?

Part-B

Answer All the following questions.


(5X10M=50Marks)

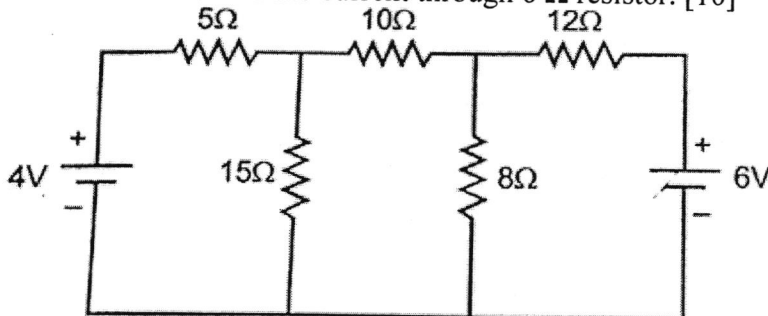- 11 Use nodal methods find the current through $8\ \Omega$ resistor. [10]



OR

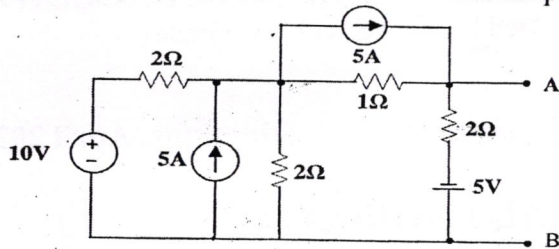- 12 Obtain the Norton equivalent circuit across points A and B for the circuit shown in fig. [10]



- 13 Three impedance $Z_1 = (17.32+j10)$, $Z_2 = (20+j34.64)$ and $Z_3 = (0-j10)$ ohms are delta connected to a 400 V, 3 Φ system. Determine the phase currents, line currents, and total power consumed by the load. [10]
- OR
- 14 Derive expression for Average and RMS value of Sine wave form. [10]
- 15 Explain the principle, construction and operation of single-phase transformer in detail with a neat diagram. [10]
- OR
- 16 Explain the principle, construction and operation of single-phase Auto transformer in detail with a neat diagram. [10]
- 17 With a neat diagram explain construction, principle and working of three phase squirrel cage Induction motor. [10]
- OR
- 18 Explain construction, principle and working of DC generator in detail with a neat diagram. [10]
- 19 Describe in detail about various types of electrical wires and cables with neat diagrams. [10]
- OR
- 20 Describe in detail about MCB and MCCB with neat diagrams. [10]