



R17 Regulation

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY  
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 1E2AE

**B.Tech I Year II Semester Supplementary Examinations, October 2022**  
**Basic Electrical and Electronics Engineering**

(Common to CE & ME)

Maximum Marks: 70

Date: 20.10.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Define the doping.
- 2 Define the n-type and p-type semiconductor.
- 3 Distinguish between ideal and practical voltage source?
- 4 Define the resonance in electric circuits?
- 5 Write down the applications of Zener diode?
- 6 Write down the diode applications?
- 7 Define the Transformer utilization factor.
- 8 Define the Efficiency.
- 9 What is pinch-off voltage for a JFET?
- 10 Draw the BJT symbol.

Part-B

Answer All the following questions.

(10M X 5=50Marks)

- 11 a) Deduce an expression for the equivalent capacitance of three capacitors connected in i) Parallel and ii) Series. Hence calculate the equivalent capacitance if three capacitors of capacitances 4, 2, and 8 micro – Farads are connected in 1) Series 2) Parallel  
If a voltage of 20V is connected, calculate the charge stored in each case. (5M)  
b) A series circuit comprising R, L and C is supplied at 230 V, 50 Hz. At resonance, the voltage across the capacitor is 500 V. The current at resonance is 2A. Determine the circuit parameters R, L and C. (5M)
- OR
- 12 a) Explain in detail the volt-ampere relationship of R, L and C elements with neat diagrams. (5M)  
b) Explain in detail about the steady state analysis of a series RL circuit with sinusoidal excitation. (5M)
  - 13 a) State and explain Superposition theorem. (5M)  
b) The Q factor of a RLC series circuit is 5 at a resonance frequency of 1 KHz. Assuming the power dissipation of 250W, when the current drawn is 1A, find the circuit parameters. (5M)
- OR
- 14 State and explain the Compensation theorem for AC Excitation. (10M)
  - 15 Draw PN junction diode and explain the V-I characteristics. (10M)

OR

- 16 Define the terms dynamic resistance of a diode and Diffusion capacitance of a diode. (10M)  
17 Compare the characteristics of L - section, capacitor and  $\pi$  -filters. (10M)

OR

- 18 Explain the Bridge rectifier with neat waveforms and derive the ripple factor and efficiency. (10M)  
19 Explain the V-I characteristics of FET. (10M)

OR

- 20 a) Draw the circuit and explain the drain and gate characteristics of a JFET. (5M)  
b) Differentiate between BJT and FET. (5M)