



**B.Tech II Semester Regular/Supplementary Examinations, October 2022**

**SEMICONDUCTOR DEVICES & CIRCUITS**  
(Common to *EEE, CSE, CSE(AI&ML), CSE(DS) and IT*)

**Maximum Marks: 70**

Date: 15.10.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

**Part-A**

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Define Doping.
- 2 What is load line analysis?
- 3 Write any two differences between Zener breakdown and Avalanche breakdown.
- 4 What is varactor diode and how does it work?
- 5 Define rectifier.
- 6 What are the types of filters?
- 7 What are the biasing conditions of a transistor to operate in active region and cut off region?
- 8 In a transistor, the base current and collector current is  $60 \mu\text{A}$  and  $1.75 \text{ mA}$  respectively. What will be the emitter current? Calculate the value of  $\alpha$  of transistor.
- 9 Why the input impedance of FET is more than that of a BJT?
- 10 Compare Depletion MOSFET and enhancement MOSFET.

**Part-B**

Answer All the following questions.

(5X10M=50Marks)

- 11 a) Discuss about ideal versus practical diode. (5 Marks)  
b) What is a Diode? Explain about the working Principle of Diode. (5 Marks)
- OR
- 12 A silicon diode is asymmetrically doped at  $N_D = 10^{19} \text{ cm}^{-3}$  and  $N_A = 10^{16} \text{ cm}^{-3}$ . (Note that at  $N_D = 10^{19}$  the semiconductor is on the edge of degeneracy, but we can assume that non-degenerate carrier statistics are close enough for this problem) Assume that the minority electron and hole lifetimes are  $\tau_n = \tau_p = 10^{-6} \text{ s}$ . The lengths of the N and P regions are  $L = 500 \mu\text{m}$  and  $L \gg x_p, x_n$ .
    - i) Estimate the applied forward bias at which the P-region enters high-level injection.
    - ii) Compute the current density at the onset of high-injection. (10 marks)

- 13 a) For the Zener diode voltage regulator with  $V_S = 20\text{ V}$ ,  $R_S = 100\ \Omega$ ,  $V_Z = 12\text{ V}$ ,  $R_L = 680\ \Omega$ , determine
- Load voltage.
  - Voltage drop across series resistance  $R_S$ .
  - Current through the Zener diode. (5 Marks)
- b) Discuss the working of a Zener diode as a voltage regulator. (5 Marks)
- OR
- 14 a) Draw the basic structure of a SCR and explain its characteristics. (5 Marks)
- b) What is varactor diode? What are the differences between a tunnel diode & an ordinary PN junction diode? (5 Marks)
- 15 a) Explain the working of Bridge rectifier. Give the expressions for RMS current, PIV, ripple factor and efficiency. (5 Marks)
- b) The applied input AC power to a half-wave rectifier is 100 watts. The DC output power obtained is 40 watts.
- What is the rectification efficiency?
  - What happens to remaining 60 watts? (5 Marks)
- OR
- 16 a) Explain the working of  $\pi$ - section Filters. (7 Marks)
- b) Why Pi filters are not suitable for varying loads? (3 Marks)
- 17 a) Distinguish between the different types of transistor configurations with necessary circuit diagrams. (5 Marks)
- b) Explain input and output characteristics of CE configuration. (5 Marks)
- OR
- 18 If the common-emitter h-parameters of a transistor are given by  $h_{ie} = 2000\ \Omega$ ,  $h_{fe} = 49$ ,  $h_{re} = 5.5 \times 10^{-4}$  and  $h_{oe} = 2.5 \times 10^{-5}$ . The source and load resistances of a CE amplifier are equal to  $2\text{ k}\Omega$ . Compute  $A_V$ ,  $R_i$  and  $R_o$ . Also find the common base h-parameters of the transistor. (10 Marks)
- 19 Explain the operation of N-Channel JFET with its characteristics and explain the different regions in transfer characteristics? (10 Marks)
- OR
- 20 Describe the construction and explain the operation of depletion mode N-Channel MOSFET. Also draw the static characteristics. (10 Marks)