



R18 Regulation

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 2P3BB

B.Tech III Semester Supplementary Examinations, March/April 2023

ELECTRICAL CIRCUIT ANALYSIS
(Electrical and Electronics Engineering)

Maximum Marks: 70

Date: 29.03.2023 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)


- 1 Discuss the ideal transformer? Write the expression for turns ratio?
- 2 Define tree and graph?
- 3 Define the time constant for series RL circuit?
- 4 Why transient occurs in electric circuits?
- 5 What is the Laplace transform of step and exponential functions?
- 6 Define poles and zeros in a transfer function?
- 7 What is a driving point in transfer function? Explain.
- 8 Define the h-parameters.
- 9 What is the significance of single tuned filters over double tuned filters?
- 10 Distinguish between the constant "k" and m-derived filters?

Part-B

Answer All the following questions.

(5X10M=50Marks)

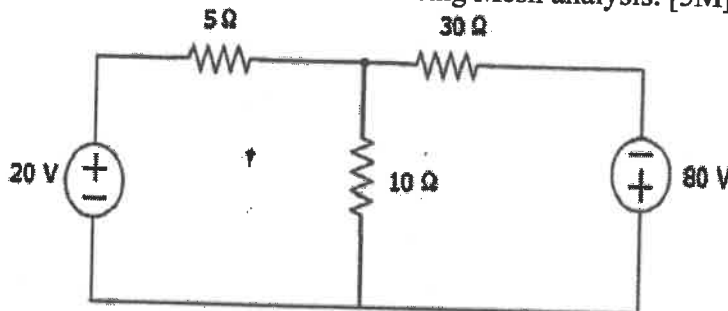
- 11 A. Find the voltage across $30\ \Omega$ resistor using Mesh analysis. [5M]



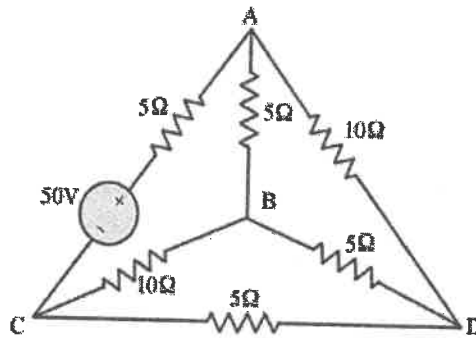
- B. Three coils connected in series-aiding fashion have a total inductance of 250mH. When connected in series opposing configurations, the coils have a total inductance of 150mH. If the inductance of one coil (L_1) is three times the other. Find L_1 , L_2 and M ? What is the coupling coefficient? [5M]

OR

- 12 For the network shown in Fig. write a tie-set schedule and then find all the branch currents and voltages. [10M]




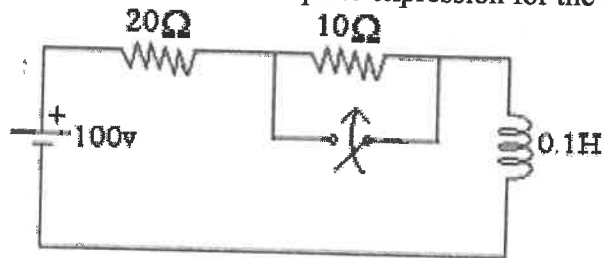- 13 A. Derive the expressions for the transient current of RL series circuit when excited by a dc voltage. [5M]
 B. A dc voltage of 100V is applied in the circuit shown in figure below and the switch is kept open. The switch K is closed at $t = 0$. Find the complete expression for the current. [5M]




OR

- 14 A. Derive the expression for the transient response in an RLC series circuit excited by a DC source. [5M]
 B. A constant voltage is applied to a series RL circuit at $t = 0$. The voltage across the inductor at $t = 3.46$ ms is 20 V and 5 V at $t = 25$ ms. Obtain R if $L = 2$ H. [5M]
- 15 A sinusoidal voltage of $105 \sin(40t)$ is applied to a series circuit of $R = 25$ and $L = 1.5$ H at $t = 0$ (shown in Figure), by Laplace transform method. Determine the current $i(t)$ for all $t = 0$. Assume zero initial conditions. [10M]

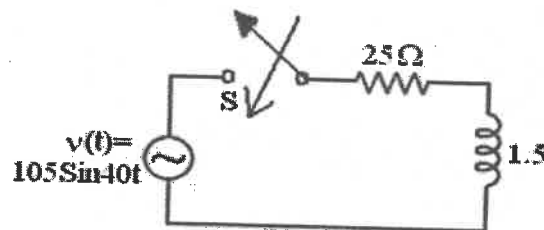


OR

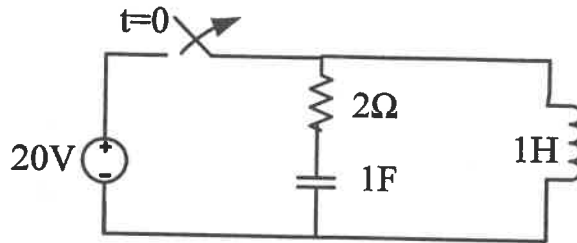- 16 A. For the circuit shown in Fig, determine the current delivered by the source when the switch is closed at $t=0$, using Laplace transformation. Assume there is no initial charge on the capacitor and no initial current through the inductor. [6M]



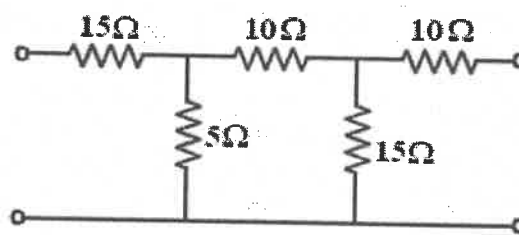B. A coil of inductance 5 mH and resistance 10 Ω is connected in parallel with a 250 nF capacitor across a 50 V variable-frequency supply. Determine (a) the resonant frequency, (b) the dynamic resistance, (c) the current at resonance. [4M]

- 17 A. Derive the relation between ABCD and 'Z'-parameters. [5M]
 B. Obtain 'Z' – parameters for the given network shown in below figure. [5M]



[5+5]

OR

- 18 A. A two-port network has the following parameters: $Z_{11} = 4 \Omega$, $Z_{12} = 1 \Omega$, $Z_{21} = 3 \Omega$ and $Z_{22} = 3 \Omega$. Calculate short circuit parameters. [5M]
 B. Explain in detail about the interconnection two-port networks? [5M]
- 19 A. List out the types of filters? And sketch the band pass filter? [5M]
 B. Discuss in detail about the design considerations of m-derived high pass filters in both T-type and π type sections? [5M]
- OR
- 20 A. Write a short-notes on composite filter design? [5M]
 B. Discuss in detail about the design considerations of constant "k" low pass and high pass filters? [5M]

