



R18 Regulation

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 2P3FC

B.Tech III Semester Supplementary Examinations, March/April 2023

DIGITAL LOGIC DESIGN
(INFORMATION TECHNOLOGY)

Maximum Marks: 70

Date:01.04.2023 Duration: 3 hours

- Note: 1. This question paper contains two parts A and B.
2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Reduce the following Boolean expressions to the indicated number of literals: $A'C' + ABC + AC'$ to three literals.
- 2 Find the complement of the following expression: $xy' + x'y$
- 3 Implement AND gate using NAND gate.
- 4 Write the truth table of Ex-Nor gate.
- 5 Draw a logic diagram for 2 to 4 decoder using NAND gates?
- 6 Draw an AND gate using 2:1 MUX.
- 7 Define Sequential circuits.
- 8 Examine with the help of a block diagram, the basic components of a Sequential Circuit?
- 9 State the RTL Logic.
- 10 What are the Logic Micro operations?

Part-B

Answer All the following questions.

(5X10M=50Marks)

- 11 Solve for 'x' [10]
 $i). (367)_8 = (x)_2$ $ii). (378.93)_{10} = (x)_8$ $iii). (B9F.AE)_{16} = (x)_8$ $iv). (16)_{10} = (100)_x$
OR
- 12 Encode the following message bits into 7-bit even parity hamming code [10]
 $a). (1001)_2$ $b). (1110)_2$
- 13 Minimize the following logic function using K-maps and realize using NAND gate. [10]
 $F(A,B,C,D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$
OR
- 14 Minimize the following in SOP and POS forms on the 4 variable k-map. [10]
 $F(A,B,C,D) = \sum m(0,2,3,8,9,10,11,12,13)$
- 15 Design 2-bit Magnitude comparator and write truth table for it. [10]
OR
- 16 Construct a 4 to 16 line decoder using 2 to 4 line decoders. [10]
- 17 Derive the characteristic equations of SR-flip-flop, D-flip-flop. [10]

- OR
- 18 Illustrate about a shift register? Can a shift register be used as a counter? If yes, explain how?
[10]
- 19 A. Distinguish between RAM and ROM.
B. Compare the PAL and PLA. [5+5]
- OR
- 20 Explain the following operations. [5+5]
i. Logic Micro operations, ii. Shift Micro operations