



R20 Regulation
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code:3P3DC

B.Tech III Semester Regular/Supplementary Examinations, March/April 2023

ELECTRONIC CIRCUIT ANALYSIS
(Electronics and Communication Engineering)

Maximum Marks: 70

- Note: 1. This question paper contains two parts A and B.
2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
3. Part B consists of 5 Units. Answer any one full question from each unit.
4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Date:29.03.2023 Duration: 3 hours

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 State Millers theorem.
- 2 What is the need for cascading?
- 3 Draw the small signal high frequency CE model of a transistor and list its elements?
- 4 Define Gain band width product.
- 5 Write the advantages of FET.
- 6 Define r_d and g_m ?
- 7 Write the advantages of negative feedback.
- 8 Define the Oscillators.
- 9 Define the Efficiency.
- 10 List out the applications of tuned amplifier.

Part-B

(5X10M=50Marks)

- Answer All the following questions.
- 11 Explain about different types of distortions that occur in amplifier circuits. 10M
OR
 - 12 Write the analysis of a CE amplifier circuit using h-parameters and derive the expression for A_i , R_i , A_v and R_o . 10M
 - 13 Analyze the expression for CE Current gain with R_L and explain the variation of frequency response with R_L using hybrid- π model. 10M
OR
 - 14 The input power to a device is 10,000W at a voltage of 1000V. The output power is 500W and the output impedance is 20Ω . Find the (a) Voltage gain in decibels (b) Power gain in decibels. 10M
 - 15 Common Source FET amplifier circuit has the following circuit parameters: $R_D = 5K\Omega$, $R_G = 10M\Omega$, $r_d = 35K\Omega$, $\mu = 50$. Determine A_V , R_i & R_o ? 10M
OR

- 16 A. Draw the small-signal model of common source FET amplifier. 5M
B. Derive expressions for voltage gain and output resistance? 5M
- 17 Derive the expression for the input resistance with feedback R_{if} and output resistance with feedback R_{of} in the case of (a) Voltage series feedback amplifier (b) Current shunt feedback amplifier. 10M
- OR
- 18 Draw the circuit and explain the principle of operation of RC phase-shift oscillator circuit. 10M
- 19 Derive the expression for maximum theoretical efficiency in the case of class B push pull amplifier. Illustrate its advantages and disadvantages? 10M
- OR
- 20 Draw the circuit diagram of a tuned amplifier. Derive expression for its voltage gain at resonance and bandwidth. 10M