



B.Tech III Semester Regular/Supplementary Examinations, March/April 2023
Network Analysis

(ECE)

Maximum Marks: 70

Date: 10.04.2023 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Define Twig and Link
- 2 List out any two properties of incidence matrix
- 3 What is natural response
- 4 Time constant of series RL circuit excited by constant DC source is 8 sec. Determine the inductance of the coil if the resistance of the circuits 2 K Ω
- 5 What is a transformed network
- 6 What is resonance. Write the condition for series resonance
- 7 Write the condition for reciprocity in Z and Y parameters
- 8 Define transfer impedance
- 9 What is single tuned filter
- 10 Define Propagation constant.

Part-B


Answer All the following questions.

(5X10M=50Marks)

- 11 (a) What are dual networks. Explain the construction of dual networks with an example 5M
(b) Explain dot convention. 5M


OR

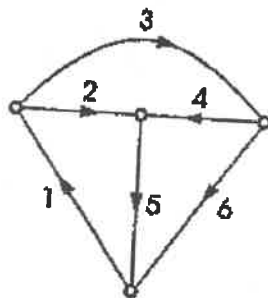- 12 Determine the tie-set matrix and tie-set schedule of the oriented graph shown below. 10M
Consider the branches of the tree as 2,4 and 5.



- 13 Derive an expression for complete response of series R-L-C circuit excited by constant DC voltage source 10M

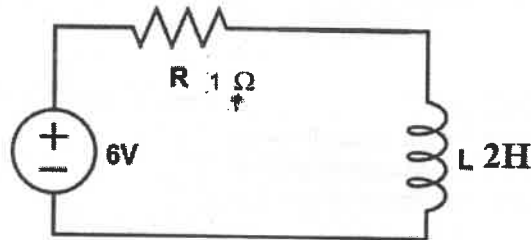- OR
- 14 Explain the transient response of series RL circuit excited by constant DC source. 10M
- 15 Determine the transient response of a series RL circuit shown in using laplace transformation when 6V source is applied at $t=0$ sec 10M



- OR
- 16 What are poles and zeros. Explain the construction of pole zero plot with an example. Explain the significance of poles and zeros 10M
- 17 (a) Explain the necessary conditions for driving point functions with suitable examples. 5M
 (b) Define the following: 5M
 (i) Reverse transfer impedance (ii) Forward Transfer admittance
- OR
- 18 Express Z parameters in terms of Y parameters. 10M
- 19 (a) Explain the design analysis of double tuned filter. 5M
 (b) Give the classification of filters. 5M
- OR
- 20 (a) Explain the analysis of low pass (LC) filter 5M
 (b) Design a high pass filter having characteristic impedance of 500Ω and cutoff frequency of 2000 Hz. 5M