



B.Tech III Semester Regular/Supplementary Examinations, March/April 2023

LOGIC CIRCUITS DESIGN
(Common to CSE & CSE(AI&ML))

Maximum Marks: 70

Date:01.04.2023 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

- 1 Convert hexadecimal E79A.6B5 to binary. (10x2M=20 Marks)
- 2 What do you mean by self complementing codes? Give examples.
- 3 Describe the importance of don't care conditions.
- 4 Implement a 16:1 mux using two 8:1 mux.
- 5 How many states do a 4 bit Johnson counter have?
- 6 What are the applications of shift registers?
- 7 What is the difference between ALU and ALSU?
- 8 What are shift micro operations?
- 9 What is the size of the decoder in a 8 x 4 ROM?
- 10 What is a combinational PLD?

Part-B

Answer All the following questions.

- 11 A. Convert the hexadecimal number 68BE to binary and then from binary convert it to octal 5M
B. Convert the following to Decimal then to Octal (125F)₁₆ b) (10111111)₂ 5M
- 12 Using Universal gates design three basic logic gates. OR 10M
- 13 Simplify the Boolean function using k-map in SOP and POS forms 10M
 $F = \sum m(0,1,2,4,7,8,12,14,15,16,17,18,20,24,28,30,31)$
- 14 What are the design steps for combinational circuits? Implement 4 input priority encoder. OR 10M
- 15 Explain Universal shift register in detail. 10M
- 16 Design synchronous mod-6 counter using clocked JK flip flops. OR 10M

- 17 Explain add and subtract operation of two signed 2's complement data. Explain the logic of each operation. 10M
- OR
- 18 Explain the hardware implementation of arithmetic logic shift unit in detail. 10M
- 19 Draw the internal logic construction of 32X4 ROM and explain how a Boolean expression is implemented using it. 10M
- OR
- 20 Implement the Boolean function $f(A,B,C)=\sum m(0,1,2,3,6)$ using PLA and PAL. 10M