



**B.Tech III Semester Regular/Supplementary Examinations, March/April 2023**  
**† Digital Logic Design**  
(IT)

**Maximum Marks: 70**

Date:01.04.2023 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

**Part-A**

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Why we need a data representation system?
- 2 Perform the conversion  $(7777)_8 = (?)_{10} = (?)_2$
- 3 For the given logic equation, implement with three NOR gates  $Y=(A+B).(C+D)$
- 4 What is k map? How it is different from truth table.
- 5 Realize OR function using 2:1 MUX
- 6 Draw the logic diagram of a one to four line demultiplexer.
- 7 Differentiate between RING and RIPPLE counter.
- 8 Why  $S=R=1$  is not permitted in SR flipflop
- 9 What is the need for state reduction in sequential circuit design?
- 10 Compare Mealy and Moore models.

**Part-B**


Answer All the following questions.

(5X10M=50Marks)

- 11 A. Perform the subtraction with the binary number  $11010 - 1101$  using  
(i) 2's complement method (ii) 1's complement method 5M  
B. Compare the BCD code and Gray code. 5M  
OR 10M
- 12 How a Hamming code locate the error? Explain with an example. 10M
- 13 A. What is Boolean algebra? How it is different from normal algebra? why it is specially suited to logic? 5M  
B. How can you get a Boolean expression from a truth table? Explain with an example. 5M  
OR
- 14 Simplify the expression by using K-Map method 10M  
 $f(A,B,C,D) = \sum m(1,2,5,6,7,9,10) + \sum d(0,13,15)$
- 15 Design 4-bit GREY to BCD code converter using logic gates. 10M  
OR
- 16 Implement a function  $F(A,B,C,D) = \sum m(0,1,3,4,8,9,15)$  using multiplexer 10M
- 17 Show the T flip flop implementation from SR flip flop and JK flip flop. 10M  
OR

18 Describe the operation of shift register. Discuss different methods of entering data into the register and reading it. 10M

19 10M

 

An input sequence 01010110100 is applied to a sequential circuit. Draw the state diagram and table then reduce it.

20 OR Explain the capabilities and limitations of FSM. 10M