



R18 Regulation *Subject code: 2P6BB*
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
 (Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech VI Semester Supplementary Examinations, July 2024

**ELECTRICAL MEASUREMENTS&INSTRUMENTATION
(EEE)**

Maximum Marks: 70

Date:22.07.2024 Duration: 3 hours

- Note: 1.This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks		(10X2M=20 Marks)	CO	Bloom Tx
1	Why scales of the gravity control instruments are not uniform but are crowded?		1	L1
2	Explain short notes on loading effect		1	L1
3	Why the secondary of a CT is never left open circuited?		2	L1
4	What are the ratios of instrument transformers?		2	L1
5	What is meant by Phantom Load?		3	L1
6	Explain overload compensation of induction type energy meter		3	L2
7	Write short notes on Owen's bridge		4	L1
8	What are the applications of Wein's bridge?		4	L1
9	Write short notes on Thermo couple?		5	L1
10	Explain the photo diodes.		5	L2

Part-B

Answer All the following questions.		(5X10M=50Marks)		
11	a) Design and explain the working of PMMC instrument. [5M] b) Write the advantages of using PMMC instrument. [5M]		1	L2
OR				
12	Explain the principle and operation of electrostatic voltmeter. [10M]		1	
13	Explain the principle and operation of basic slide wire D.C potentiometer. What is standardization of D.C potentiometer. [10M]		2	L2
OR				
14	Explain the briefly Drysdale polar type A.C potentiometer. Explain measurement of self-reactance of coil. [10M]		2	L2
15	Explain extension of range of wattmeter using instrument transformer. [10M]		3	L2
OR				
16	Explain the measurement of active and reactive powers in balanced and unbalanced system. [10M]		3	L2

17	Compare Maxwell bridge with Hay's bridge. [10M]	4	L6
	OR		
18	Evaluate the equation of balance of a Schering Bridge. Draw the phasor diagram under null conditions and explain how loss angle of capacitor can be calculated. [10M]	4	L5
19	Explain Strain gauge and its principle of operation. [10M]	5	L2
	OR		
20	Explain photovoltaic and photo conductive cells. [10M]	5	L2