



B. Tech VII Semester Regular/Supplementary Examinations, December 2024

**FLEXIBLE AC TRANSMISSION SYSTEMS
(EEE)**

Maximum Marks: 70

Date:30.12.2024

Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks		(10X2M=20 Marks)	CO	Bloom Tx
1	State Two economic benefits of using FACTS controllers.		1	BL-1
2	How do FACTS devices contribute to renewable energy integration?		1	BL-1
3	What is power oscillation damping, and why is it needed?		2	BL-1
4	How do hybrid VAR generators combine the benefits of variable impedance and switching converters?		2	BL-2
5	Which device, SVC or STATCOM, offers faster response time, and why?		3	BL-1
6	How does SVC improve voltage stability in a power system?		3	BL-1
7	What is the function of GTO thyristor in a GSC?		4	BL-1BL-1
8	Define the term series voltage injection as applied to SSSC.		4	BL-2
9	List the components of a UPFC.		5	BL-1
10	How is the voltage stability index affected by IPFC?		5	BL-2

Part-B

Answer All the following questions.		(5X10M=50Marks)	CO	Bloom Tx
11	A. Explain the dynamic stability considerations of an interconnected transmission system. [5M] B. List and discuss different types of FACTS controllers. Give examples for each type and mention their applications. [5M]		1	BL-3
OR				
12	A. Explain the Single phase full-wave bridge converter with necessary waveforms. [6M] B. Enumerate the relative merits and demerits of current source converters over voltage source converters. [4M]		1	BL-3
13	A. Explain midpoint voltage regulation for line segmentation using shunt compensation. [5M] B. Discuss the improvement of voltage stability using shunt compensation. [5M]		2	BL-3

	OR		
14	Explain how equal area criterion helps to evaluate effectiveness of shunt compensation and other flow control techniques on transient stability improvement [10M]	2	BL-3
15	A. Explain the STATCOM with smart grids. [5M] B. Explain with a neat block diagram general control scheme of Static Var Compensator (SVC TSC-TCR). [5M]	3	BL-3 BL-3
	OR		
16	Write a comparison between STATCOM and SVC in the following [10M] (i) V-I characteristics (ii) transient stability.	3	BL-3
17	A. Enumerate the basic operating control schemes of TSSC and TCSC. [5M] B. Discuss the effect of series capacitive compensation on transmission lines. [5M]	4	BL-4
	OR		
18	Explain the basic circuit arrangement and working of Static Synchronous series compensator (SSSC). [10M]	4	BL-3
19	A. Discuss the features of UPFC. [5M] B. Describe the mathematical representation of IPFC and how it manages reactive power flow across multiple transmission lines. [5M]	5	BL-3
	OR		
20	Explain the modeling of UPFC, focusing on its series and shunt components. [10M]	5	BL-3