



B.Tech I Semester Regular Examinations, March/April 2023
Electrical Circuits
(EEE)

Maximum Marks: 60

Date:06.04.2023 Duration: 3 hours

- Note: 1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x1M=10 Marks)


1. a Define Ohm's law.
- b Define Kirchoff laws.
- c Define RMS value.
- d Define quality factor.
- e State the Superposition theorem.
- f State Tellegan's theorem
- g Write the relationship between phase voltage and line voltage in a balanced star connected system?
- h List out the merits of 3-phase system over 1-phase system.
- i Define self-inductance.
- j Define tree and link.

Part-B

Answer All the following questions.


(10M X 5=50Marks)

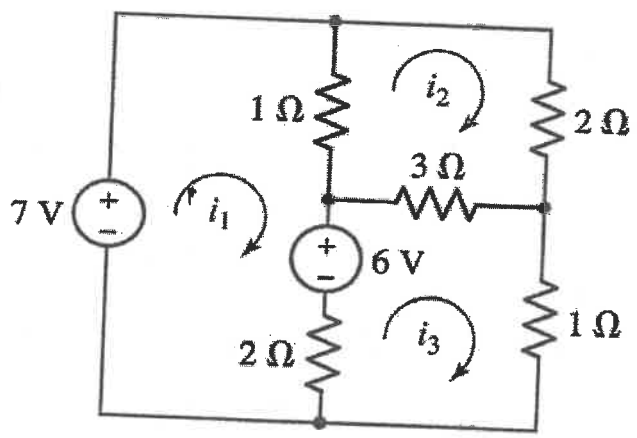- 2 A. Write the voltage current relationship for R,L,C elements. [5]
 B. Determine the current flowing through 3Ω resistance using mesh analysis in the circuit shown below: [5]



OR

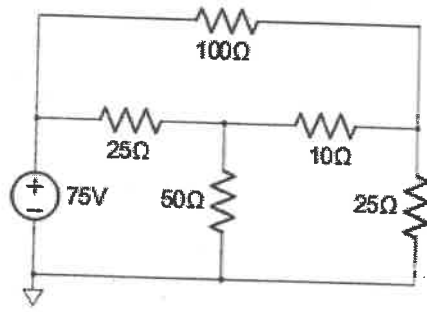- 3 Determine the current through 50 Ω resistor using nodal analysis: [10]




- 4
- A. Define form factor. Derive an expression for formfactor of a sinusoidal voltage waveform. [5]
 B. A series RLC circuit with $R = 100\Omega$ and $L=100\text{mH}$ is excited by single phase $230\text{V}, 50\text{Hz}$ sinusoidal ac supply. Determine the total impedance, current, active power and power factor of the circuit. [5]

OR


- 5
- A. Define Resonance and explain about parallel resonance. [5]
 B. Derive an expression for bandwidth of a series RLC circuit. [5]

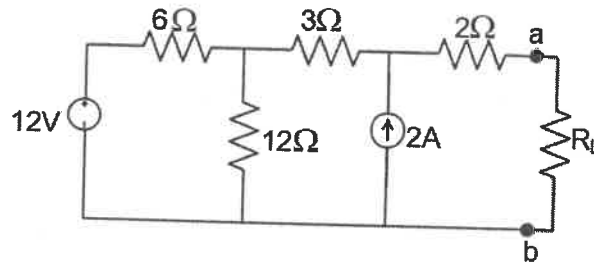- 6
- A. State and explain Norton's Theorem. [5]
 B. Determine the maximum power that can be transferred to the load resistance R_L for the circuit shown below: [5]



OR

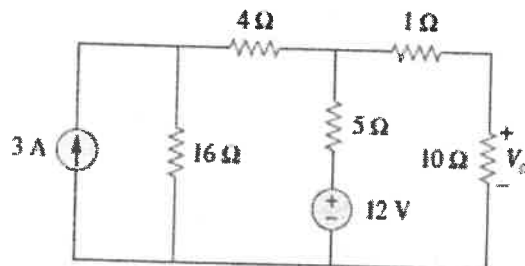- 7
- A. State and explain Millman's theorem. [5]
 B. Determine the current through 10Ω resistance using Thevenin's theorem: [5]



- 8
- A three phase balanced delta connected load of $(10+j8)$ ohm is connected across a $400\text{V}, 3-\phi$ balanced supply. Determine the phase currents and line currents. Assume phase sequence to be RYB. Also calculate the power drawn by the load. [10]

OR

- 9 Derive the relation between the line and phase quantities in star and delta connection system for a balanced star and delta connected load. [10]
- 10 Two coupled coils with $L_1=0.02\text{H}$ and $L_2=0.01\text{H}$ and $k=0.5$ are connected in series aiding, series opposing, parallel adding and parallel opposing. What are the four equivalent inductances. [10]
- OR
- 11 Define coefficient of coupling. Derive an expression for it in terms of self and mutual inductances. [10]

