



Regulation R18

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code:2E2AJ

B.Tech II Semester Supplementary Examinations, September 2023

BASIC ELECTRICAL ENGINEERING

(Common to ECE & CSE)

Maximum Marks: 70

Date:22.09.2023 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Distinguish between i) conductor ii) semiconductor iii) insulator
- 2 Define ideal voltage and current source.
- 3 What is polar form and rectangular form?
- 4 Define i) form factor ii) peak factor
- 5 Define superposition theorem.
- 6 Define Tellegen's theorem.
- 7 Write the difference between core and shell type transformers?
- 8 State Fleming's Right Hand Rule?
- 9 How you decide what size of electrical wire do you need?
- 10 List the types of cables.

Part-B

Answer All the following questions.

(5X10M=50Marks)


- 11 Explain derivation of delta-star conversion equations?

10M

OR

- 12 Calculate the current in 20 ohm resistor in the circuit shown below

10M

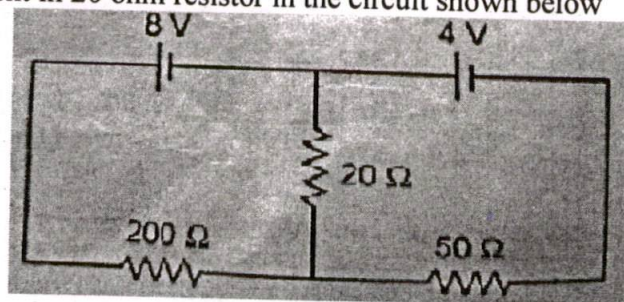

- 13 Define average value of an alternating quantity. Obtain the relation between average value and the maximum value of an alternating quantity.


10M

OR

- 14 A voltage $V=141 \sin\{314t+\pi/3\}$ is applied to i) resistor of 20Ω ii) Inductance of 0.1 henry iii) capacitance of $100\mu F$ Find in each case rms value of current and power dissipated.

10M

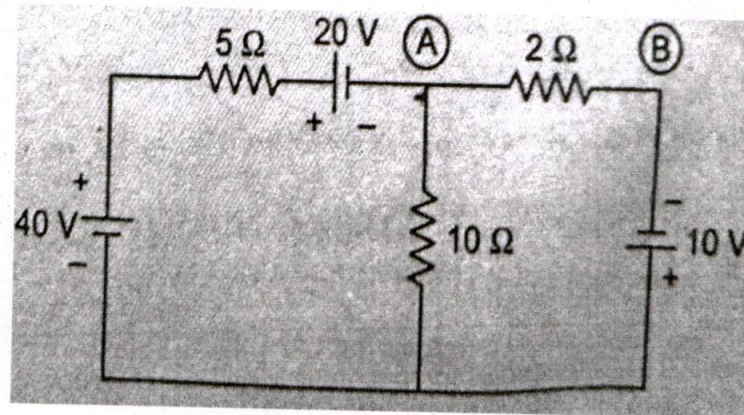- 15 Using superposition theorem, calculate current flowing in branch A-B for the circuit 10M shown



OR

- 16 State and explain millman's theorem and mention limitations of millman's theorem 10M
- 17 Derive the equation for induced EMF of a DC generator? 10M
- OR
- 18 Explain the principle of operation of transformer and losses. 10M
- 19 Explain the different types of MCB'S in details 10M
- OR
- 20 a) Explain about meter board and distribution board in detail. 5M
- b) Write short notes on Earthing? 5M