



R20 Regulation
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code:3B1AK

B.Tech I Semester Supplementary Examinations, September 2023
ELECTRONIC DEVICES

(Electronics and Communication Engineering)

Maximum Marks: 70

Date:30.09.2023 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Write the applications of P-N diode
- 2 Define Diffusion current and Drift current
- 3 Draw the symbol of Zener diode and write its applications.
- 4 Mention the applications of Tunnel Diode and Varactor diode.
- 5 Write the differences between HWR and FWR
- 6 Define the Terms PIV, Ripple factor and Efficiency of a rectifier.
- 7 Explain early effect in a transistor and Thermal runaway
- 8 Define stability factor & derive expression 'S'.
- 9 List the advantages of FET over BJT.
- 10 Draw the symbols of P-Channel JFET and N-Channel JFET.

Part-B

Answer All the following questions.

(10M X 5=50Marks)

11. Explain forward and reverse bias characteristics of P-N junction diode. (10M)
- OR
12. Derive the Diode current equation of a PN junction diode. (10M)
 13. Explain the operation of a Tunnel Diode using Energy band diagrams. (10M)
- OR
- 14.a Explain V-I characteristics of Zener diode with neat diagrams. (5M)
 - 14.b Explain how Zener diode works as a Voltage regulator (5M)

15. Explain the operation of a Full wave Rectifier. Derive its ripple factor, Efficiency, PIV. (10M)
- OR
16. Explain the operation of a half wave Rectifier. Derive its ripple factor, Efficiency, PIV, and Form Factor. (10M)
17. Explain the input and output characteristics of CB configured transistor circuit with a neat circuit diagram. (10M)
- OR
18. Explain the self - bias technique of a Transistor and derive its stability factor. (10M)
19. With the help of neat circuit diagram explain the operation of N- channel JFET. (10M)
- OR
20. Explain the construction and operation of a Depletion MOSFET and draw its characteristics (10M)