



R20 Regulation

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code:3E2AN

B.Tech II Semester Supplementary Examinations, September 2023

BASIC ELECTRICAL ENGINEERING
(Common to ECE,CSE,CSE(AI&ML),CSE(DS) and IT)

Maximum Marks: 70

Date:22.09.2023 Duration: 3 hours

- Note:
- 1.This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Define Kirchoff's voltage law and current law.
- 2 Discuss Faradays law of electromagnetic induction.
- 3 Modify the following rectangular quantities into polar.
a) $20+j30$ (b) $5-j10$
- 4 Show the relationship between line values and phase values of voltage and current in star and delta connection.
- 5 State Thevenin's theorem.
- 6 State the Millman's theorem.
- 7 Classify armature windings a in DC machine.
- 8 Differentiate ideal transformer and practical transformer.
- 9 Write the importance of earthing.
- 10 Classify the types of wires.


Part-B

Answer All the following questions.

(5X10M=50Marks)


- 11 Build the expression for star – delta transformations 10M
OR
- 12 Derive the expression for self inductance, mutual inductance and coefficient of coupling of magnetic circuit. 10M
- 13 Derive the expression for average value, RMS value, Form factor and Peak factor of sinusoidal waveform. 10M
OR
- 14 Outline the resonance of series RLC circuit and derive expressions for resonance frequency, quality factor and bandwidth. 10M

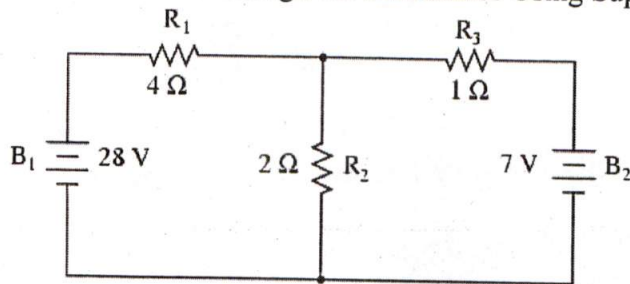- 15 Measure current through the 2Ω resistor Using Superposition Theorem. 10M



OR

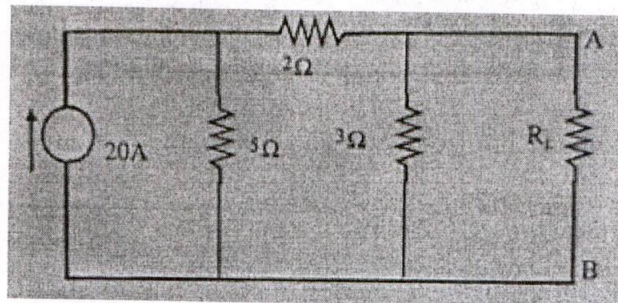- 16 The circuit shown in the figure R_L absorbs maximum power. Compute the value of R_L and maximum power. 10M



- 17 A. Analyze principle of operation of DC generator. 5M
 B. Show the expression for torque equation of DC motor. 5M
- OR
- 18 Analyze the equivalent circuit of single phase transformer. outline its equivalent circuit applications. 10M
- 19 Summarize the function of circuit breaker and describe about MCB, ELCB and MCCB. 10M
- OR
- 20 Classify the types of batteries and mention the important characteristics of batteries. 10M
 Recommend type of battery for domestic appliances