



Regulation R22

Subject code:4E1AE

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

B.Tech I Semester Supplementary Examinations, September-2023 ELECTRICAL CIRCUITS

(EEE)

Maximum Marks: 60

Date:30.09.2023 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x1M=10 Marks)

- 1.a State Ohm's Law.
- b State KVL and KCL.
- c Define Resonance and Resonant frequency.
- d Define the term form factor, peak factor and Time period.
- e Write the statement of Superposition theorem
- f Write the statement of Thevenin's theorem
- g Draw the Phasor diagram for AC through series RL circuit
- h What is complex power
- i Define self-Inductance
- j Define connected and unconnected graph?

Part-B


Answer All the following questions.

(5X10M=50Marks)

- 2 Derive the voltage, current, power and energy equations for Resistor, Inductor and 10M Capacitor.

OR

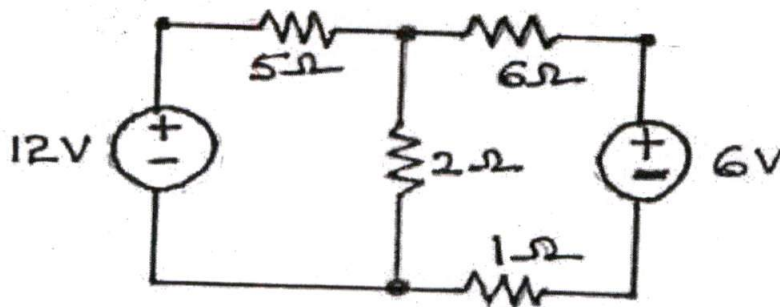- 3 Determine the current through all resistors using mesh method for the network given below 10M




- 4 A voltage wave represented by $V=200\sin 314t$ find 10M
 - i) Maximum value
 - ii) Average value
 - iii) RMS value
 - iv) Frequency

5 Define Apparent power, Active power and Reactive power and also draw the power triangle 10M


OR

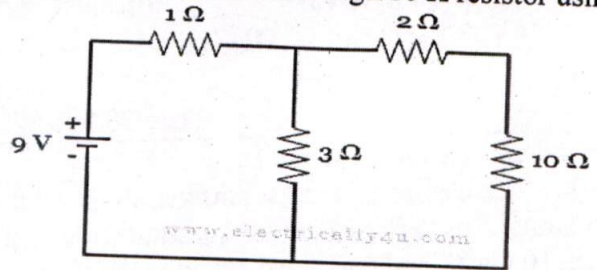6 For the given circuit, determine the current through 10 Ω resistor using Norton's theorem 10M



OR

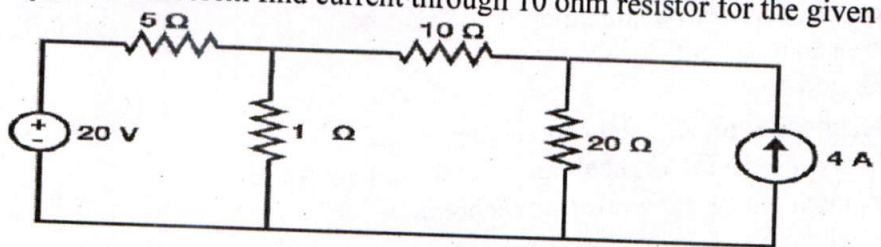7 Using superposition Theorem find current through 10 ohm resistor for the given circuit. 10M




8 A three-phase balanced delta connected load of $(10+j8)$ ohm is connected across a 400V, 3-φ balanced supply. Determine the phase currents and line currents. Assume phase sequence to be RYB. Also calculate the power drawn by the load. 10M

OR

9 Derive the relation between the line and phase quantities in star and delta connection system for a balanced star and delta connected load. 10M

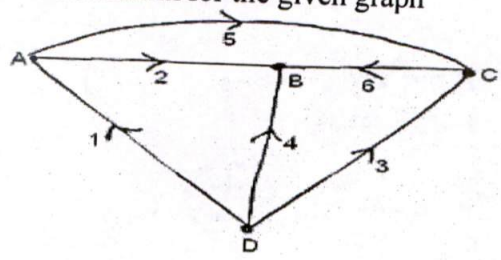10 Develop the fundamental tie-set matrix for the given graph 10M



OR

11 Derive an expression of self and Mutual inductance for the Magnetically Coupled circuits 10M