



**R20 Regulation**  
**TKR COLLEGE OF ENGINEERING AND TECHNOLOGY**  
 (Autonomous, Accredited by NAAC with 'A+' Grade)

Subject code: 3P3BC

**B.Tech III Semester Supplementary Examinations, February 2024**  
**ANALOG ELECTRONICS**

(EEE)

Maximum Marks: 70

Date: 21.02.2024 Duration: 3 hours

- Note: 1. This question paper contains two parts A and B.  
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.  
 3. Part B consists of 5 Units. Answer any one full question from each unit.  
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

**Part-A**

All the following questions carry equal marks

(10X2M=20 Marks)

|    |                                                              | CO  | Bloom Tx |
|----|--------------------------------------------------------------|-----|----------|
| 1  | What are the types of distortion in amplifiers?              |     |          |
| 2  | What are the advantages of h-parameter model in transistors? | CO1 | L1       |
| 3  | Compare the negative feedback and positive feedback          | CO1 | L1       |
| 4  | State Barkhausen criterion for oscillation                   | CO2 | L3       |
| 5  | What is thermal runaway?                                     | CO2 | L1       |
| 6  | Mention the advantages of push pull power amplifiers.        | CO3 | L1       |
| 7  | Distinguish between shunt clippers and series clippers.      | CO3 | L2       |
| 8  | Define clamping circuit theorem.                             | CO4 | L3       |
| 9  | How transistor can be used as a switch.                      | CO4 | L1       |
| 10 | Compare astable and bistable multivibrators.                 | CO5 | L1       |
|    |                                                              | CO5 | L3       |

**Part-B**

Answer All the following questions.

(5X10M=50Marks)

|    |                                                                                                                                          |     |     |    |
|----|------------------------------------------------------------------------------------------------------------------------------------------|-----|-----|----|
| 11 | Draw the h-parameter equivalent circuit for typical common emitter amplifier and derive expression for $A_i$ , $A_v$ , $R_i$ and $R_o$ . | 10M | CO1 | L4 |
|    | OR                                                                                                                                       |     |     |    |
| 12 | A. Define and explain the parameters transconductance $G_m$ , drain resistance $R_d$ and amplification factor of JFET.                   | 5M  | CO1 | L2 |
|    | B. Compare CE, CE and CC configurations in property wise.                                                                                | 5M  |     | L3 |
| 13 | A. What are the advantages and disadvantages of negative feedback in Amplifiers. Explain.                                                | 5M  | CO2 | L2 |
|    | B. Draw the block diagram of voltage series feedback amplifier and derive the expression for Input and output resistance from it.        | 5M  |     | L3 |
|    | OR                                                                                                                                       |     |     |    |
| 14 | Describe the construction of RC phase shift oscillator and explain its working.                                                          | 10M | CO2 | L4 |

|    |                                                                                                                                                                                                   |          |     |          |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|-----|----------|
| 15 | A. Explain the transformer coupled amplifier with neat diagrams.<br>B. Compare Push Pull Class -B and Complimentary symmetry class - B power amplifiers.                                          | 5M<br>5M | CO3 | L2<br>L2 |
|    | OR                                                                                                                                                                                                |          |     |          |
| 16 | Show that the Transformer coupled Class -A Amplifier maximum efficiency is 50%.                                                                                                                   | 10M      | CO3 | L3       |
| 17 | A. Draw the Low pass RC circuit and explain its output response for pulse and ramp inputs.<br>B. Draw the circuit of a clipping at two independent levels using diodes and explain its operation. | 5M<br>5M | CO4 | L3<br>L2 |
|    | OR                                                                                                                                                                                                |          |     |          |
| 18 | A. How to clip the input signal above the reference level by using Shunt diode clipper.<br>B. State and prove Clamping circuit theorem.                                                           | 5M<br>5M | CO4 | L2<br>L2 |
| 19 | Draw and explain the working principle of A stable multivibrator and derive frequency of oscillations                                                                                             | 10M      | CO5 | L3       |
|    | OR                                                                                                                                                                                                |          |     |          |
| 20 | A. Write short notes on switching times of Transistor.<br>B. What is the use of Schmitt trigger ? Explain its operation.                                                                          | 5M<br>5M | CO5 | L2<br>L2 |