



B.Tech III Semester Supplementary Examinations, July 2024

**ELECTRICAL CIRCUIT ANALYSIS
(EEE)**

Maximum Marks: 70

Date:20.07.2024 Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks (10X2M=20 Marks)		CO	Bloom Tx
1	State Thevenin's Theorem?	1	L2
2	Define Tree and Co-tree?	1	L1
3	What is the main reason for the transients to occur in a circuit?	2	L1
4	Explain transient conditions for the inductor and capacitor?	2	L1
5	Define Bandwidth and selectivity?	3	L1
6	Define the term form factor, peak factor and Time period?	3	L2
7	Give the Laplace transform for the signal step, ramp, Impulse and sine inputs?	4	L1
8	What is pole-zero plot?what is its significance	4	L1
9	Explain the symmetry condition for ABCD and Y parameters	5	L1
10	Draw the Equivalent circuit of Y-Parameter and write the equations?	5	L2


Part-B


Answer All the following questions. (5X10M=50Marks)

11	Explain Basic incidence matrix and Basic cut set matrix with an example? (10M)	1	L2
----	--	---	----

OR

12	Write the statement of Norton's theorem (10M) Draw the Norton's equivalent circuit and find the current through 5ohm resistance across the terminal A-B of the circuit shown below.	1	L3
----	--	---	----

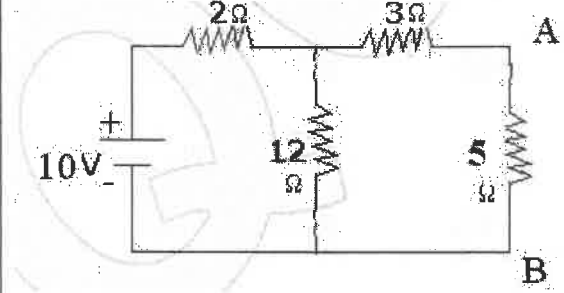

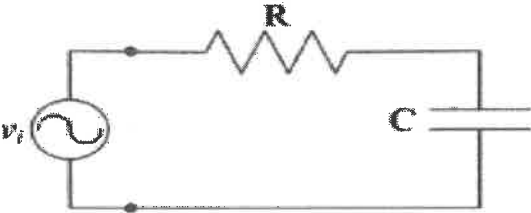13	<p>a) Derive the Transient state response for Current in first order RL series circuit. (5M)</p> <p>b) Define: (5M)</p> <p>(i) Order of circuit?</p> <p>(ii) Forced Response & Natural Response?</p> <p>(iii) Time constant for series RL and RC circuits</p>	2	L3
OR			
14	<p>a) Derive the expression for Current $i(t)$ for a parallel RL Circuit (5M)</p> <p>b) Derive the expression for Current $i(t)$ for a Series RC Circuit (5M)</p>	2	L3
15	<p>For the RLC series circuit $R=5\text{ohms}$, $L=0.03\text{H}$, $C=100\text{ micro farads}$. (Determine the Frequency at which the circuit resonates. Also find the quality factor, voltage across the inductance, voltage across capacitance, at resonance (10M)</p>	3	L3
OR			
16	<p>Derive the resonance condition for series and parallel RLC circuits with neat waveform. (10M)</p>	3	L3
17	<p>Analyse the series RL circuit using laplace transform when a unit step input is applied. (10M)</p>	4	L2
OR			
18	<p>a) Find the initial and final value of the function whose Laplace transform is $H(S)=20/(S + 3)(S^2+8S+25)$ (5M)</p> <p>b) Using Laplace Transform find the current $i(t)$ in the below circuit. (5M)</p>	4	L2
			
19	<p>Derive the condition of Reciprocity and symmetry for a two port transmission. (10M)</p>	5	L3
OR			
20	<p>In the given network as shown in Fig. Find Z – parameters and check the conditions for symmetry and Reciprocity. X (10M)</p>	5	L3
