



R20 Regulation *Subject code: 3P3DC*
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
(Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech III Semester Supplementary Examinations, July 2024

**ELECTRONIC CIRCUIT ANALYSIS
(ECE)**

Maximum Marks: 70

Date: 20.07.2024 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks (10X2M=20 Marks)		CO	Bloom Tx
1	List the various possibilities of inter-stage coupling of amplifiers.	1	L1
2	Draw the circuit diagram of Darlington amplifier	1	L1
3	Define the gain bandwidth product of common emitter amplifier in terms of high frequency parameters	2	L1
4	Define the following (i) $r_{b'e}$ (ii) r_{bb}	2	L2
5	Compare different MOS amplifiers	3	L2
6	What are the advantages and disadvantages of negative feedback	3	L2
7	What are the conditions for sustained oscillations or what is Barkhausen criterion	4	L3
8	State the frequency for RC phase shift oscillator.	4	L3
9	What is thermal runaway?	5	L4
10	What are different types of tuned amplifiers?	5	L4

Part-B

Answer All the following questions. (5X10M=50Marks)			
11	a) Draw the circuit diagram of a common Emitter amplifier along with its equivalent circuit by using approximate analysis. Derive expressions for A_v , R_i , A_i and R_o . (5M) b) What is non-linear distortion? List the causes for this type of distortion in amplifiers. (5M)	1	L3
OR			
12	Draw the circuit for Cascode Amplifier. Explain its working, obtaining overall values of the circuit in terms of h-parameters. (10M)	1	L3
13	Derive the expression for the CE current gain A_i with resistive load in hybrid π model. (10M)	2	L3
OR			
14	a) Prove that (i) $h_{fe} = g_m * r_{b'e}$ for a Hybrid π model of CE amplifier (5M)	2	L4

	b) Derive the expression for the CE short current gain A_i in hybrid π model. (5M)		
15	Explain the Analysis of CG JFET Amplifier. (10M) OR	3	L4
16	Explain the Analysis of CD JFET Amplifier. (10M)	3	L3
17	Derive the expression for the input resistance with feedback R_{if} and output resistance with feedback R_{of} in the case of (10M) (a) Voltage series feedback amplifier. (b) Voltage shunt feedback amplifier OR	4	L4
18	a) Differentiate between RC and LC type oscillators. (5M) b) Derive the expression for frequency of oscillation in a Wein bridge Oscillator. (5M)	4	L2
19	In a class B complementary power amplifier $V_{cc}=+15V$, $-V_{cc}=15V$ and $R_L=4\Omega$. Calculate: (i) Maximum a.c power which can be developed (ii) Collector dissipation while developing maximum a.c power (iii) Efficiency (iv) Maximum power dissipation per transistor (10M) OR	5	L3
20	Draw the circuit and explain the working principle of a complementary symmetry push-pull power amplifier and state its disadvantages? (10M)	5	L2