



R22 Regulation

Subject code: 4E3BC

# TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech III Semester Supplementary Examinations, July 2024

## ANALOG ELECTRONICS

(EEE)

Maximum Marks: 60

Date: 23.07.2024 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

### Part-A

All the following questions carry equal marks		(10X1M=10 Marks)	CO	Bloom Tx
1.a)	What is the difference between Clipping and Clamping		1	1
b)	How BJT act as switch		1	1
c)	Draw the structure of p-channel JFET?		2	2
d)	Define pinch off voltage?		2	1
e)	What is the use of the heat sink in power amplifiers		3	1
f)	Define Q factor.		3	1
g)	What are the conditions for oscillation?		4	1
h)	Classify the various negative feedback amplifiers		4	2
i)	Draw the pin diagram of $\mu A741$ .		5	2
j)	Define slew Rate		5	1

### Part-B

Answer All the following questions.		(5X10M=50Marks)		Bloom Tx level
2	A. Explain in detail about the junction diode switching times. [5]		1	2
	B. With neat sketch explain the working and construction of NPN transistor. [5]		1	2
OR				
3	A. For any transistor amplifier, Prove that $R_i = (h_i / 1 - h_r A_v)$ . [5]		1	1
	B. With a neat sketch, explain the working of negative clamper. [5]		1	1
4	Explain the analysis of CS FET amplifier. [10]		2	2
OR				
5	A. Compare the performance of BJT and FET amplifiers. [5]		2	3
	B. Discuss the analysis of CD JFET amplifier. [5]		2	2
6	Draw the class-A transformer coupled power amplifier and explain its operation and derive the equation for its efficiency and explain its working. [10]		3	4
OR				

7	A. Design a class B power amplifiers to deliver 25w to a load resistor $R_L=8\text{ohms}$ , using transformer coupling. $V_m=V_{cc}=25\text{V}$ . Assume necessary data. [5]	3	3
	B. Derive the equation for efficiency class B push pull power amplifier. [5]	3	4
8	A. Show that the bandwidth increases in negative feedback amplifiers. [5]	4	3
	B. Discuss about Frequency and amplitude stability of oscillators. [5]	4	2
	OR		
9	A. Derive the expression for frequency of oscillation of Hartley oscillator. [5]	4	1
	B. Derive the expression for input and output resistance of voltage series feedback amplifier with a neat diagram. [5]	4	1
10	A. Explain the operation of a practical integrator with suitable mathematical expressions. [5]	5	2
	B. Write a technical note on frequency response characteristics of Differential amplifier. State the importance of frequency compensation. [5]	5	1
	OR		
11	Explain various DC and AC characteristics of an op.amp. [10]	5	2