



R22 Regulation Subject code: 4E3DC
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
 (Autonomous, Accredited by NAAC with 'A+' Grade)
B.Tech III Semester Supplementary Examinations, July 2024

NETWORK THEORY
 (ELECTRONICS & COMMUNICATION ENGINEERING)

Maximum Marks: 60

Date: 23.07.2024 Duration: 3 hours


- Note: 1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks (10X1M=10 Marks)		CO	Bloom Tx
1.a)	Define a connected graph.		
b)	Define tree of an electric network with example.	CO1	2
c)	Write down the few applications of RL, RC, RLC circuits.	CO1	2
d)	What is meant by transient response?	CO1	1
e)	List two conditions that a time-domain function must satisfy for its Laplace Transform to exist.	CO2	2
f)	Distinguish between Laplace transform and Inverse Laplace transform	CO2	2
g)	Find the Z Parameters For The Two Port Network In Fig.1	CO3	2
<p>Figure.1</p>			
h)	Provide one example of how two-port networks are used in telecommunications systems.	CO3	1
i)	Define the Q-factor of a filter.	CO4	2
j)	Why impedance matching is important in filter design.	CO4	2

Part-B

Answer All the following questions. (5X10M=50Marks)			Bloom Tx level
2	The graph of a network is shown in Fig. Write the a) Tieset matrix, b) Cutset matrix. Consider branches (4), (5) and (6) as tree branches. [10]	CO1	3

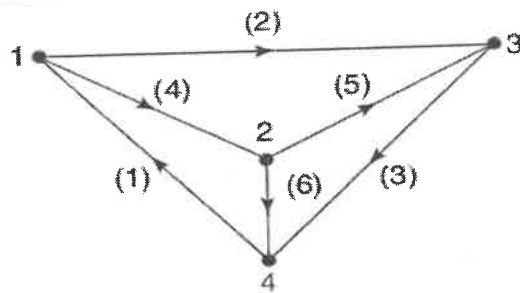

Figure

OR

3 Find the dual network of the network shown in figure. [10]

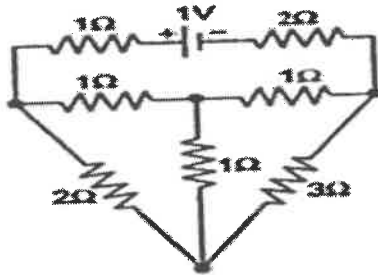


Figure.

4 Determine whether RLC series circuit shown in Figure is under damped, overdamped, or critically damped. Also, find $V_L(0^+)$, di/dt at 0^+ and $i(\infty)$ [10]

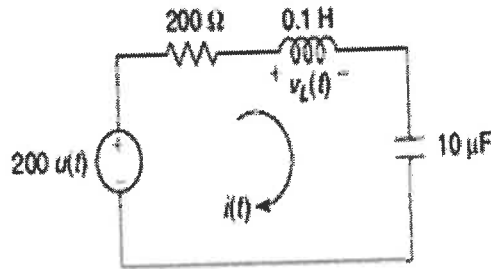


Figure.

OR

5 a) Derive the expression for voltage across capacitance of a parallel R -C excited with a sinusoidal current source at $t=0$. [5]
 b) Simple RL series circuit excited by a sinusoidal source. The circuit is initially relaxed At $t=0$ the switch is closed. Find the response $i(t)$ for the circuit. [5]

6 Find the inverse Laplace transform of the function. [10]
 $F(s) = (3s + 2)/(s^2 + 4s + 5)$

OR

7	<p>In the circuit shown in figure. the switch is moved from 1 to 2 at time $t = 0$. The steady-state current having previously established in the R-L circuit, find the expression for the current $i(t)$ after switching using Laplace transform method. [10]</p>	CO2	4
<p>Figure.</p>			
8	<p>Calculate the transmission parameters of the network shown below Figure. Also verify the Reciprocity & symmetricity of the network. [10]</p>	CO3	3
<p>Figure .</p> <p style="text-align: center;">OR</p>			
9	<p>Obtain the Y parameters for the circuit shown below figure. [10]</p>	CO3	3
<p>Figure</p>			
10	<p>a) Enlist limitation of passive filters. [5] b) Design a m-derived high pass filter with a cut – off frequency of 10KHz; design impedance of 5Ω and $m=0.4$. [5]</p>	CO4	4
OR			
11	<p>a) What is the purpose of using filters in electronic circuits, and how do they contribute to signal processing. [5] b) Discuss the characteristics and frequency response of a single-tuned filter. [5]</p>	CO4	2

