



R18 Regulation

Subject code: 2E1AD

**TKR COLLEGE OF ENGINEERING AND TECHNOLOGY**

(Autonomous, Accredited by NAAC with 'A+' Grade)

**B.Tech I Semester Supplementary Examinations, June 2024**

**BASIC ELECTRICAL ENGINEERING**  
(Common to CE,EEE,ME & IT)

Maximum Marks: 70

Date:05.07.2024 Duration: 3 hours

- Note:
- 1.This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks (10X2M=20 Marks)

Q.NO	QUESTIONS	CO	Blooms Tx
1	State Ohm's law.	CO1	L1
2	State Norton's theorem.	CO1	L1
3	Define time period.	CO1	L1
4	Define i) form factor ii) peak factor	CO1	L1
5	Define transformation ratio.	CO2	L1
6	Write the iron losses of the transformers?	CO2	L2
7	Define motor.	CO3	L1
8	Write the Emf equation of a dc generator?	CO3	L1
9	Write about Earthing?	CO4	L2
10	List the types of cables.	CO4	L1


Part-B

Answer All the following questions. (10M X 5=50Marks)

11	State Kirchoff's voltage law and Kirchoff's Current law with suitable example. [10M]	CO1	L2
----	--	-----	----

OR

12	Find the current response across 3Ω resistor using superposition theorem. [10M]	CO1	L3
----	---	-----	----

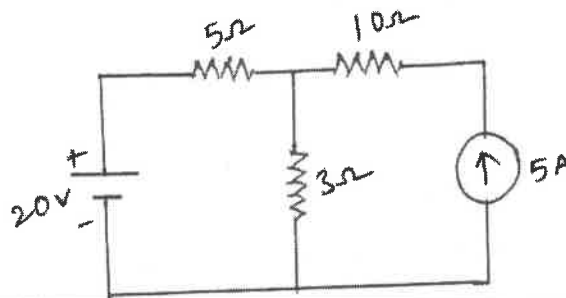

13	Explain following terms: [2MX5=10M] i) form factor ii) peak factor iii) phase difference iv) frequency v) Power factor ?	CO1	L2
OR			
14	Derive the expression for impedance (Z), phase angle ( $\Theta$ ) and power factor ( $\cos\phi$ ) for RLC series circuit with relevant phasors. [10M]	CO1	L3
15	Explain the principle of operation of transformer and derive the Emf equation. [10M]	CO2	L2
OR			
16	Explain about Auto-Transformer with neat diagram. [10M]	CO2	L2
17	Explain the constructional features of DC machine with neat diagram. [10M]	CO3	L3
OR			
18	Explain the working of 3-phase induction motor. [10M]	CO3	L2
19	Explain the different types of MCB'S in details. [10M]	CO4	L2
OR			
20	Classify the types of batteries and mention the important characteristics of batteries. [10M]	CO4	L2