



R20 Regulation *Subject code: 3E2AH*
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
 (Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech II Semester Supplementary Examinations, June 2024

SEMICONDUCTOR DEVICES AND CIRCUITS
(Common to EEE, CSE, CSE(AI&ML), CSE(DS) & IT)

Maximum Marks: 70

Date 28.06.2024 Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A			
All the following questions carry equal marks		(10X2M=20 Marks)	Blooms Tx
1	What is doping.	L1	C1
2	Define static and dynamic forward resistances.	L1	C1
3	Define Zener breakdown.	L1	C2
4	Draw V-I characteristics of SCR.	L1	C2
5	Define PIV, Peak factor and Ripple factor of a rectifier.	L1	C3
6	Draw the circuit of Bridge rectifier with capacitor filter.	L2	C3
7	Write the relation between α , β and γ .	L6	C4
8	Define stability factor.	L6	C4
9	List the advantages of FET over BJT.	L1	C5
10	Draw the symbols of P-Channel JFET and P-Channel enhancement MOSFET	L1	C5
Part-B			
Answer All the following questions.		(5X10M=50Marks)	
11.a	Explain how depletion layer is formed in P-N junction Diode with neat diagrams. (7M)	L2	C1
11.b	Determine the value of forward current for a pn junction with $I_o = 15 \mu A$, $V_f = 0,6V$, at $T=300K$. Assume silicon diode. (3M)	L3	C1
OR			
12.a	Derive current equation of a diode. (6M)	L6	C1
12.b	Derive the expression for Dynamic resistance. (4M)	L6	C1
13.	Explain the operation of a Tunnel Diode using Energy band diagrams. (10M)	L2	C2
OR			
14	Explain the V-I Characteristics of Zener diode with neat sketches. (10M)	L2	C2

15.a	Draw the circuit and explain the operation of a Bridge Rectifier. (7M)	L2	C3
15.b	A sinusoidal voltage whose $V_m=20V$ is applied to Full wave bridge Rectifier. The diode may be considered to be ideal and $R_L=1K\Omega$ is connected as load. Find out the peak current, DC current, RMS current and ripple factor. (3M)	L3	C3
OR			
16.	Draw and explain the operation of full wave rectifier with L-section filter. (10M)	L2	C3
17.	Explain the input and output characteristics of CE configured transistor circuit with a neat circuit diagram. (10M)	L2	C4
OR			
18.a	Explain operating point of a transistor and explain the concept of D.C Load line. (7M)	L2	C4
18.b	Determine the operating point for a fixed bias circuit whose $V_{cc}=10V$, $R_c=2K\Omega$, $R_b=930K\Omega$, $\beta=50$ for a silicon transistor. (3M)	L3	C4
19.	With the help of neat circuit diagram explain the operation of N-channel JFET. (10M)	L4	C5
OR			
20.	Explain the construction and operation of a Depletion MOSFET and draw its characteristics. (10M)	L2	C5