



B.Tech I Semester Supplementary Examinations, June 2024
Electrical Circuits
 (EEE)

Maximum Marks: 60

Date: 27.06.2024 Duration: 3 hours



- Note:**
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks		(10X1M=10 Marks)	CO	Bloom Tx
1.	a	Differentiate ideal and practical sources.	1	BL1
	b	Two inductors with inductances of 3H and 6H are connected in parallel. Determine the equivalent inductance.	1	BL3
	c	A sinusoidal source is represented by $v(t)=300\sin 314t$. Determine the peak value and frequency of the waveform.	2	BL3
	d	Define Frequency.	2	BL4
	e	Write the statement of reciprocity theorem.	3	
	f	State the superposition theorem.	3	BL3
	g	Write the relationship between line voltage and phase voltage and line current and phase current in a balanced star connected system.	4	BL2
	h	Define Active power	4	BL4
	i	Define co-tree.	5	BL1
	j	Define self-inductance.	5	BL1

Part-B

Answer All the following questions.		(5X10M=50Marks)		
2	a)	Explain about active and passive elements. [5]	1	BL3
	b)	Explain about Kirchoff current and voltage law. [5]		
OR				
3	Determine i_x in the circuit shown below. [10]		1	BL2
4	A. Determine the form factor and RMS value of sinusoidal voltage.		2	BL4

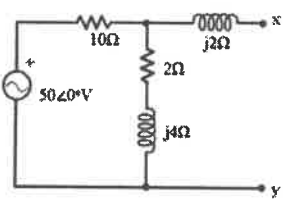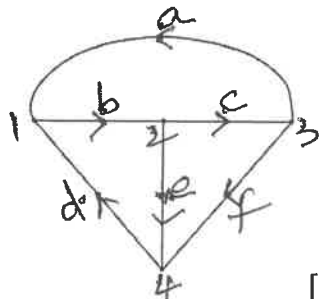	B. A series RLC circuit with $R=20\Omega$, $L=0.H$ and $C = 100\mu F$ is excited by single phase 230V,50Hz ac source. Determine (i) Impedance of the circuit (ii) Current (iii) Power (iv) Power factor of the load [5+5]		
	OR		
5	Define Resonance and find the Resonance frequency of series RLC circuit [10]	2	BL1
6	State and explain the Nortons theorem with a suitable example. [10]	3	BL2
	OR		
7	A. State and explain Superposition theorem. B. Determine the Thevenin's equivalent circuit across the terminals X-Y in the circuit shown below.  [5+5]	3	BL4
8	Prove that two watt meters are sufficient to measure the total 3-phase active power in a 3-phase circuit. Derive an expression for power factor in terms of wattmeter readings. [10]	4	BL2
	OR		
9	A. Derive the relationship between line and phase quantities of current and voltage in a balanced delta connected system. B. A three-phase 415V,50Hz source is supplying power to a balanced three-phase delta connected load of $8+j6 \Omega$. Determine the line current power and power factor of the load. [5+5]	4	BL4
10	What is dot convention. Explain the self-inductance and mutual inductance [10]	5	BL3
	OR		
11	A. Define Graph, tree and Branch. B. Determine the cut-set matrix for the graph shown in figure. Consider the branch of tree as b, c and e.  [5+5]	5	BL4