



R18 Regulation

Subject code:2P3DE

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech III Semester Supplementary Examinations, December 2024

PULSE AND DIGITAL CIRCUITS (ECE)

Maximum Marks: 70

Date:11.12.2024

Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

| All the following questions carry equal marks (10X2M=20) Marks) | | CO | Bloom Tx |
|---|--|----|----------|
| 1 | Draw the low pass RC circuit. | 1 | L1 |
| 2 | Write the condition of RC circuit to work as differentiator. | 1 | L1 |
| 3 | What are the clipping circuits? | 2 | L1 |
| 4 | What do you mean by a regenerative comparator? | 2 | L1 |
| 5 | Define storage time and transition time of a diode. | 3 | L1 |
| 6 | Define the terms slope error and transmission error. | 3 | L1 |
| 7 | What are the types of triggering? | 4 | L1 |
| 8 | Define the resolving time and resolution time. | 4 | L1 |
| 9 | Write the principle of sampling gates. | 5 | L1 |
| 10 | Define Positive and Negative logic systems. | 5 | L1 |

Part-B

| Answer All the following questions. (5X10M=50Marks) | | CO | Bloom Tx |
|---|---|----|----------|
| 11 | What is an attenuator? How can an uncompensated attenuator be modified as a compensated attenuator. Give the comparison between perfect compensation, under compensation and over compensation. [10M] | 1 | L2 |
| OR | | | |
| 12 | Explain the operation of RLC series and parallel circuits. [10M] | 1 | L2 |
| 13 | Classify different types of clipper circuits. Draw their circuits and explain their operation and also transfer characteristics. [10M] | 2 | L2 |
| OR | | | |
| 14 | A) What do you mean by biased clamping? [5M] B) A 100V peak square wave with an average value of 0V and a period of 20ms is to be negatively clamped at 25V. Draw the input and output waveforms and necessary circuit diagram. [5M] | 2 | L2 |
| 15 | A) Write a short notes on diode switching times. [5M] | 3 | L2 |

| | | | |
|----|---|---|----|
| | B) With the help of neat diagram, explain the working of two diode sampling gate. [5M] | | |
| | OR | | |
| 16 | With the help of a neat circuit diagram, explain the working of a transistor Current time base generator. [10M] | 3 | L2 |
| 17 | What is Monostable Multivibrator? Explain the principle of operation of a monostable multivibrator with the help of neat circuit diagram. [10M] | 4 | L2 |
| | OR | | |
| 18 | With the help of neat circuit diagram and waveform, explain the principle of operation of astable multivibrator. [10M] | 4 | L2 |
| 19 | Describe the working of a 6-Diode sampling gate with necessary diagram & equations. [10M] | 5 | L2 |
| | OR | | |
| 20 | Draw the circuit diagram of a positive 3 i/p NAND gate in DTL logic and explain its working. [10M] | 5 | L2 |