



Indian In Character • Innovation in Education

B.Tech III Semester Regular/Supplementary Examinations, December 2024

Network Theory (ELECTRONICS & COMMUNICATION ENGINEERING)




Maximum Marks: 60

Date: 06.12.2024

Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A		CO	Bloom Tx
All the following questions carry equal marks (10X1M=10 Marks)			
1.a)	Define Graph.	1	1
b)	Define Basic Tie set.	1	1
c)	Define the time constant of RL circuit.	2	1
d)	Define transient responses. Give one example	2	1
e)	State the Laplace transform of ramp function.	3	1
f)	State the Laplace transform of impulse function.	3	1
g)	Define impedance parameters.	4	1
h)	Define Hybrid parameters.	4	1
i)	What is high pass filter?	5	1
j)	Define propagation constant.	5	1
Part-B		CO	Bloom Tx
Answer All the following questions. (5X10M=50Marks)			
2	Explain the steps to obtain Basic Cut set in detail. [10M]	1	3
OR			
3	Develop the dual of the given network [10M]	1	3
4	Illustrate an expression for current response of RL series circuit transients. [10M]	2	3
OR			
5	The switch in Figure below has been closed for a long time it opens at $t=0$ solve $i(t)$ for $t>0$ [10M]	2	3

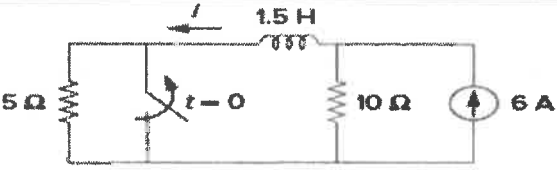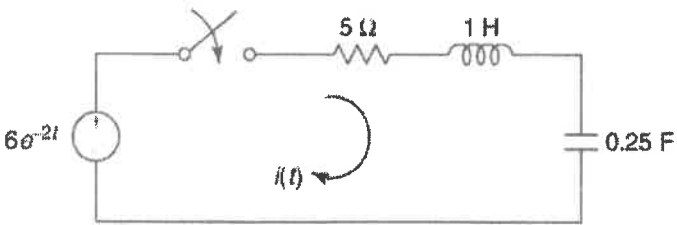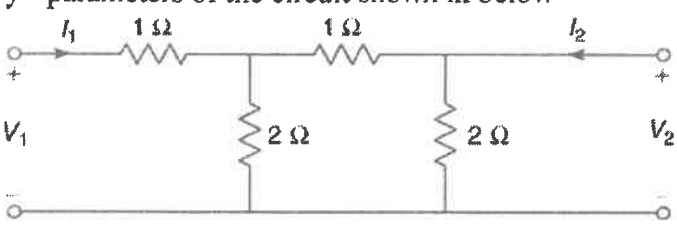			
6	<p>For the network shown in figure below the switch is closed at $t = 0$. Determine the current $i(t)$ by Laplace transform Approach Assuming Zero initial conditions [10M]</p> 	3	3
OR			
7	<p>Solve the inverse Laplace transform of function $H(s) = \frac{4}{(s+1)(s+3)}$ [10M]</p>	3	3
8	<p>Determine y - parameters of the circuit shown in below [10M]</p> 	4	3
OR			
9	<p>Compare the relation between z and h parameters? [10M]</p>	4	5
10	<p>Summarize briefly about single tuned filters. [10M]</p>	5	5
OR			
11	<p>Compare different types of filters with neat sketches along with their advantages. [10M]</p>	5	5