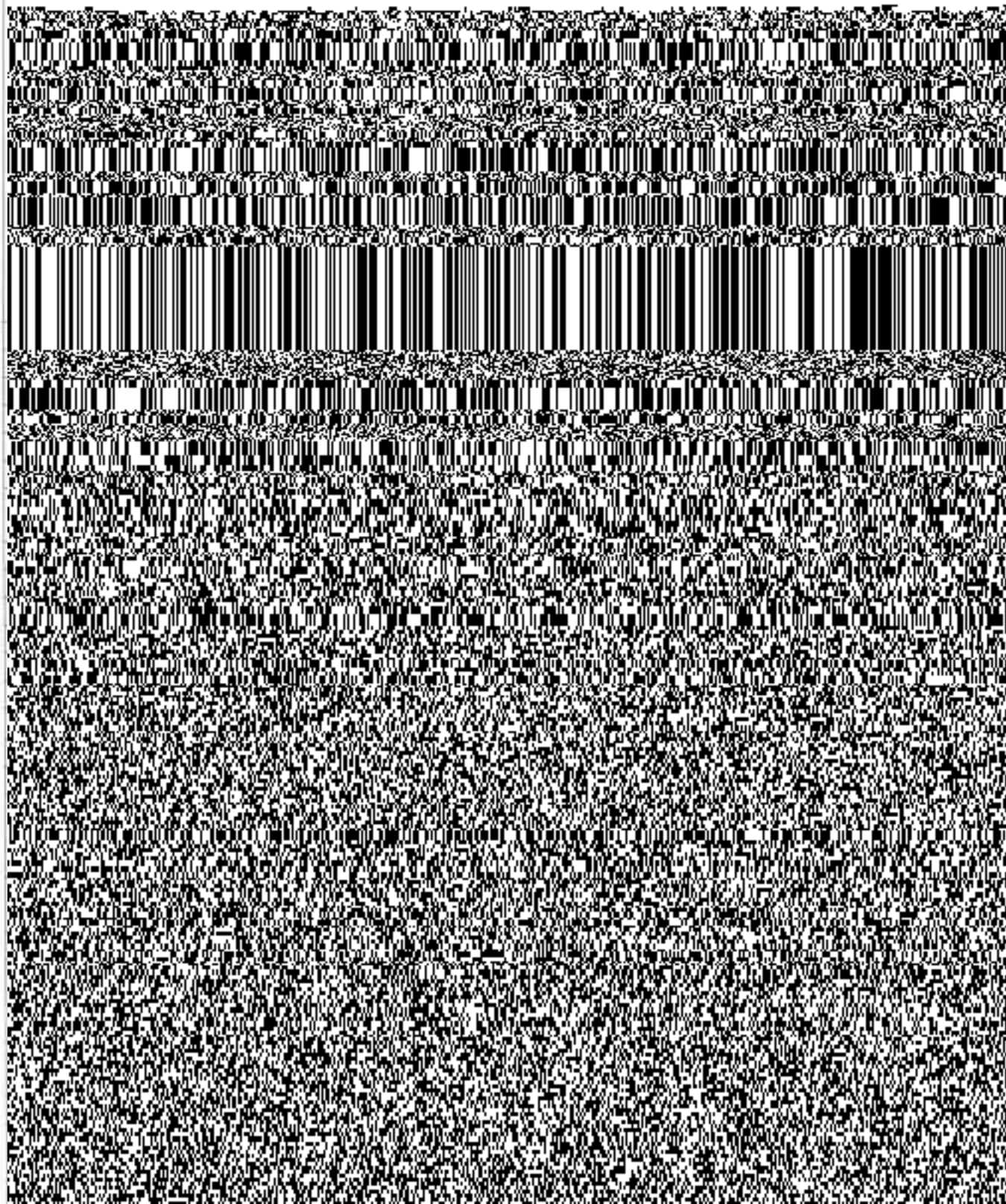




	OR			
18	Distinguish between small signal and large signal amplifiers. How are the power amplifiers classified? Describe their characteristics.	10M	4	L2
19	Sketch & describe the working of clipping circuits a) series diode positive clipper circuit b) series diode negative clipper circuit	10M	5	L2
	OR			
20	Explain the transistor switching times.	10M	5	L2