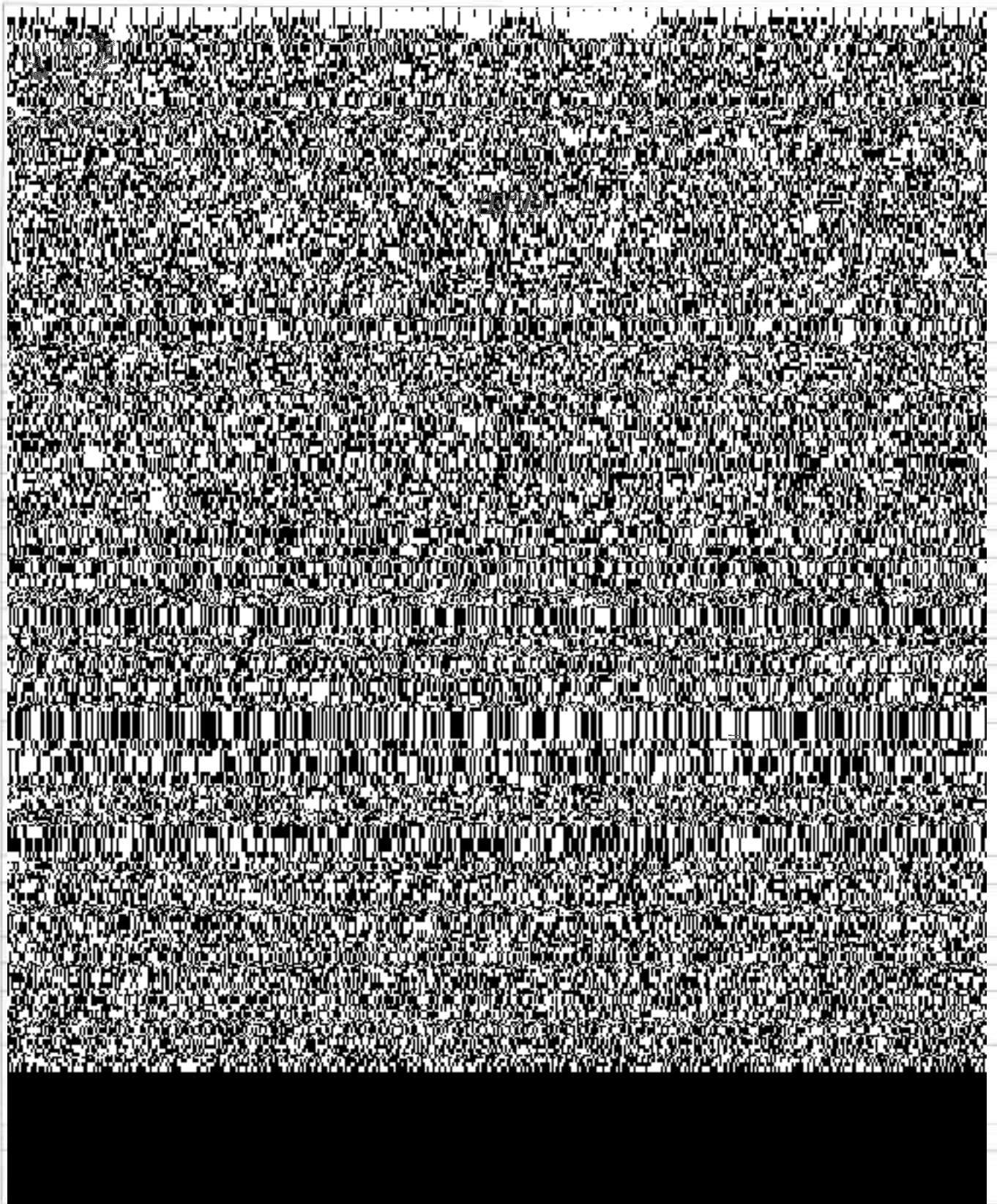




17	Explain the Operation of Class B Push-Pull Amplifier and derive maximum Power Efficiency.	10M	4	L2
	OR			
18	Compare the characteristic features of Direct coupled, Resistive Capacitor coupled, and Transformer coupled amplifiers.	10M	4	L2
19	Explain Class A Power Amplifier and derive Overall Efficiency.	10M	5	L2
	OR			
20	Explain Single tuned and Double tuned Amplifiers.	10M	5	L2