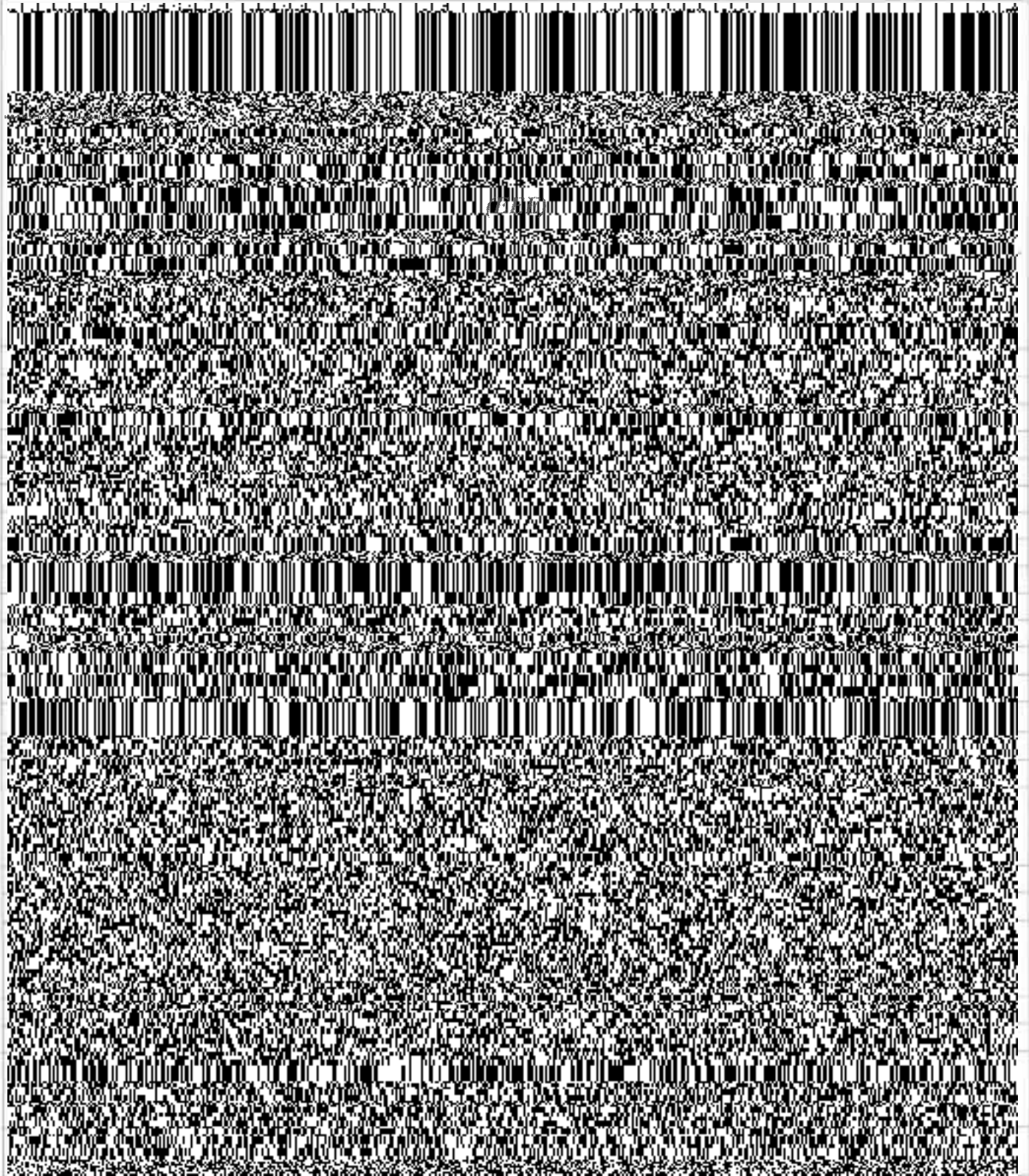




OR

9	Describe the construction of RC phase shift oscillator and explain its working.	10M	4	L3
10	Discuss about output offset voltage, input bias current and input offset current of Op-amp.	10M	5	L3
	OR			
11	Draw the integrator diagram using op-amp and explain its operation.	10M	5	L2