



R18 Regulation

Subject code:2P5DB

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech V Semester Supplementary Examinations, November 2025

VLSI DESIGN

(ECE)

Maximum Marks: 70

Date: 20.11.2025

Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

| All the following questions carry equal marks (10X2M=20 Marks) | | Marks | CO | BTL |
|--|--|-------|----|-----|
| 1 | What is body effect? | 2M | 1 | L1 |
| 2 | Define figure of merit. | 2M | 1 | L1 |
| 3 | Explain different MOS layers. | 2M | 2 | L1 |
| 4 | What is stick diagram? | 2M | 2 | L1 |
| 5 | List the sources of wiring capacitance. | 2M | 3 | L1 |
| 6 | Define Switch logic. | 2M | 3 | L1 |
| 7 | What are different types of Serial Access Memories | 2M | 4 | L1 |
| 8 | Draw the circuit diagram of full adder. | 2M | 4 | L1 |
| 9 | Write the abbreviation of FPGA. | 2M | 5 | L1 |
| 10 | Define controllability. | 2M | 5 | L1 |

Part-B

| Answer All the following questions. (5X10M=50Marks) | | Marks | CO | BTL |
|---|---|-------|----|-----|
| 11 | With neat sketches explain CMOS fabrication in an n-well process. | 10M | 1 | L2 |
| OR | | | | |
| 12 | Explain the operation of NMOS enhancement transistor. | 10M | 1 | L2 |
| 13 | Sketch the schematic, stick diagram and layout for the Boolean expression $Y = (AB + C)'$. | 10M | 2 | L2 |
| OR | | | | |
| 14 | Draw the CMOS logic circuit, stick diagram and layout for the following Boolean expression $F = [A.(B+C)]'$. | 10M | 2 | L2 |
| 15 | What are the alternate gate circuits available? Explain any one of them with suitable sketch by taking NAND gate as an example. | 10M | 3 | L2 |
| OR | | | | |
| 16 | What are the issues involved in driving large capacitive loads in VLSI circuits? Explain. | 10M | 3 | L2 |
| 17 | Draw the basic circuit diagram of static RAM cell and explain its read and write operation. | 10M | 4 | L2 |

| | | | | |
|----|--|----------|---|----|
| | OR | | | |
| 18 | a) Explain about serial access memories. b) Explain about different types of ROM. | 5M 5M | 4 | L2 |
| 19 | Explain the architecture of FPGA with neat diagram. | 10M | 5 | L2 |
| | OR | | | |
| 20 | Discuss chip level testing techniques. | 10M | 5 | L2 |