



| | |
|----|--|
| OR | |
| 12 | Derive the expression for self inductance, mutual inductance and coefficient of coupling of magnetic circuit. [10M] |
| 13 | Define average value of an alternating quantity. Obtain the relation between average value and the maximum value of an alternating quantity. [10M] |
| OR | |

| | |
|----|--|
| 14 | A voltage $V=141 \sin\{314t+\pi/3\}$ is applied to i) resistor of 20Ω ii) Inductance of 0.1 henry iii) capacitance of $100\mu\text{F}$. calculate in each case rms value of current and power dissipated . [10M] |
| 15 | i) Examine Tellegan's theorem for DC excitation with an example. [5M] ii) Determine the current I in the branch AB of circuit shown in figure-4 by using Norton's Theorem. [5M] |
| | |
| OR | |
| 16 | i) Analyze Reciprocity Theorem for AC excitation with an example. [5M] ii) Illustrate Thevenin's equivalent circuit for the circuit shown in below Figure-5. [5M] |
| | |
| 17 | Explain the constructional parts of dc machine with a neat diagram. [10M] |
| OR | |
| 18 | Design the equivalent circuit of single-phase transformer referred to the primary side. [10M] |
| 19 | Summarize the concept of wiring system and Earthing. [10M] |
| OR | |
| 20 | Examine the importance of power factor improvement and the important characteristics of batteries. [10M] |