



B.Tech I Semester Regular/Supplementary Examinations, January 2025

ELECTRICAL CIRCUITS (EEE)

Maximum Marks: 60

Date:31.01.2025

Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A


All the following questions carry equal marks		(10X1M=10 Marks)	CO No.	Bloom Tx
1.	a Define Network.		1	1
	b Define KCL.		1	1
	c What is average value?		2	1
	d Define Q Factor.		2	1
	e State the Super position theorem.		3	1
	f What is the condition for maximum power transfer theorem?		3	1
	g List one advantage of balanced 3-phase system.		4	1
	h Draw the circuit for 3-phase 4 wire system star connected system.		4	1
	i Define Mutual Inductance.		5	1
	j What is incident matrix?		5	1



Part-B

Answer All the following questions.		(5X10M=50Marks)		
2	A. In detailed explain about active and passive elements with examples. [5M] B. Recall the concept of source transformation and explain briefly. [5M]		1	3 3

OR

3	A. What is mesh analysis brief the step-by-step procedure? [5M] B. Determine the current in 10Ω resistor for the following network by using nodal analysis. [5M]		1	3 3
---	---	--	---	--------

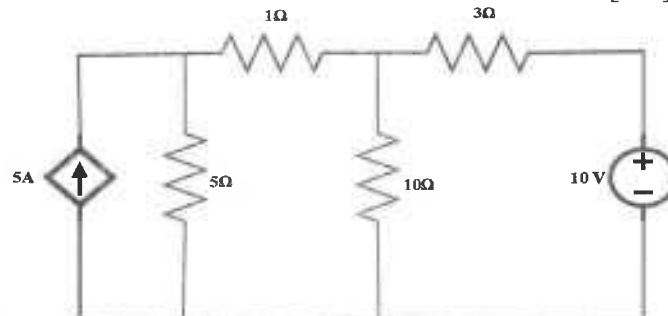

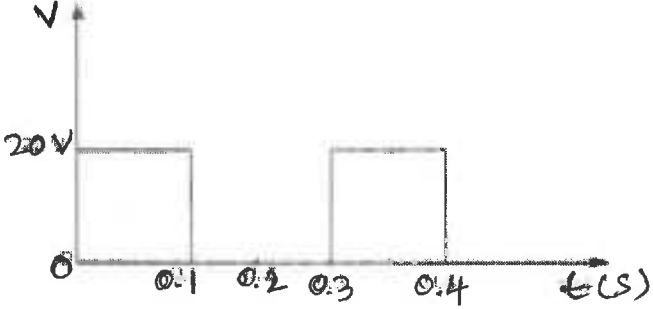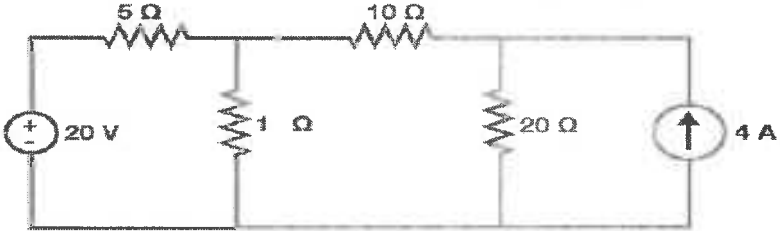4	<p>A. Evaluate the average value of square wave form depicted below. [5M]</p>  <p>B. Write short notes on steady state response of RL series circuit. [5M]</p>	2	3
OR			
5	<p>A. Explain about Quality factor and Band-width of Series resonance. [5M]</p> <p>B. Analysis of RC series circuits describe in brief. [5M]</p>	2	3
6	<p>Verify superposition Theorem and find current through 10 ohm resistance for the given circuit. [10M]</p> 	3	3
OR			
7	<p>State Thevenin's theorem and solve with an example and draw its equivalent circuit. [10M]</p>	3	3
8	<p>Balanced Y-connected load of 10 kW at 0.8 power factor lagging supplied by a 50-Hz, 300-V, three-phase system. Find the line current delivered by the source. Draw the phasor diagram. [10M]</p>	4	3
OR			
9	<p>Explain in detailed about the measurement of three-phase power using two watt meter method. [10M]</p>	4	3
10	<p>Derive an expression of self and Mutual inductance for the Magnetically Coupled circuits. [10M]</p>	5	3
OR			
11	<p>Explain the following with examples (i) Graph (ii) tree (iii) Basic cut set (iv) Basic tie set? [10M]</p>	5	3