



R22 Regulation

Subject code:4E2AG

**TKR COLLEGE OF ENGINEERING AND TECHNOLOGY**

(Autonomous, Accredited by NAAC with 'A+' Grade)

**B.Tech II Semester Regular/Supplementary Examinations, July 2025**

**NETWORK ANALYSIS**

(EEE)

Maximum Marks: 60

Date: 11.07.2025

Duration: 3 hours



- Note: 1. This question paper contains two parts A and B.  
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.  
 3. Part B consists of 5 Units. Answer any one full question from each unit.  
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks (10X1M=10 Marks)		Marks	CO	BTL
1.a	Define time constant of series R-L circuit.	1M	1	1
b	What is natural response?	1M	1	1
c	Draw and represent an exponential voltage function with magnitude V.	1M	2	2
d	Draw the voltage response curve for a Parallel R-L circuit for step current.	1M	2	2
e	What is Laplace transformation of a ramp signal having a magnitude of V.	1M	3	2
f	What is Laplace transformation of the function $\sin \omega t$ ?	1M	3	3
g	What is the condition for reciprocity in Z parameters?	1M	4	1
h	Which parameters are used to analyze parallel connected two-port networks.	1M	4	2
i	What is constant K filter?	1M	5	1
j	Define attenuation constant $\alpha$ .	1M	5	2

Part-B

Answer All the following questions. (5X10M=50Marks)		Marks	CO	BTL
2	a) Derive an expression for complete response of a series R-L circuit excited by constant DC Voltage source. b) Find the expression for capacitor voltage $v_0(t)$ if the switch is closed at $t=0$ sec. Assume switch was open for long time. <div style="text-align: center;"> </div>	5M 5M	1	3
OR				
3	Derive an expression for transient response of series R-L-C circuit for constant DC excitation. Draw the response curves.	10M	1	1

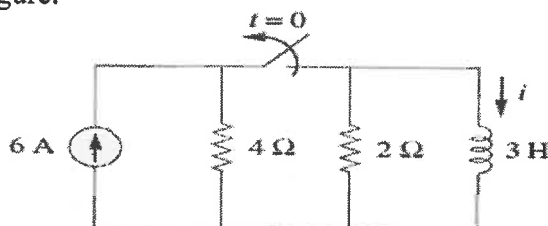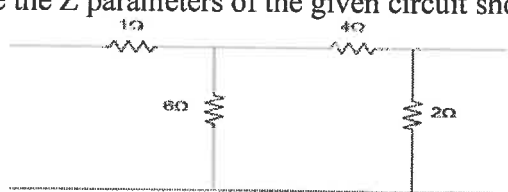4	<p>a) Explain transient response of parallel R-C circuit.  b) Determine the expression for inductor current for <math>t &gt; 0</math> sec in the circuit shown in figure.</p> 	5M 5M	2	2
OR				
5	Derive an expression for transient voltage of Parallel R-L-C circuit excited by step voltage.	10M	2	1
6	Define transient response. Derive an expression for transient response of series R-C circuit excited by step voltage using Laplace transformation.	10M	3	2
OR				
7	Determine the expression for inductor current for $t > 0$ sec in the circuit shown in figure below using Laplace transformation. Determine the time constant of the circuit.	10M	3	4
OR				
8	<p>a) Determine the Z parameters of the given circuit shown below</p>  <p>b) Express Y parameters in terms of h parameters.</p>	5M 5M	4	3
OR				
9	Derive an expression for overall Z parameters when two-port networks are connected in series.	10M	4	1
10	<p>a) What is filter. Give classification of filters  b) Design a constant K low pass filter with cut-off frequency of 3KHz and nominal impedance of 600Ω.</p>	5M 5M	5	3
OR				
11	Explain M derived low pass filter operation and design procedure.	10M	5	2