



R22 Regulation

Subject code:4E3EA

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech III Semester Regular/Supplementary Examinations, December 2025

SEMICONDUCTORS DEVICES AND CIRCUITS

(Common to CSE, CSE(AI&ML) & CSE(DS))

Maximum Marks: 60

Date: 30.12.2025

Duration: 3 hours

- Note: 1. This question paper contains two parts A and B.
2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
3. Part B consists of 5 Units. Answer any one full question from each unit.
4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

Table with 5 columns: Question, Marks, CO, BTL. Contains 10 sub-questions (1.a-j) regarding semiconductor properties and devices.

Part-B

Table with 5 columns: Question, Marks, CO, BTL. Contains 4 main questions (2-5) regarding diode characteristics and Zener diode applications.

	OR			
5	With the help of energy band diagrams explain the operation and characteristics of Tunnel Diode.	10M	2	3
6	A sinusoidal voltage whose $V_m=26V$ is applied to half-wave rectifier. The diode may be considered to be ideal and $R_L=1.2 K\Omega$ is connected as load. Find out peak value of current, RMS value of Current, DC value of current and Ripple factor.	10M	3	
	OR			
7	a) Derive the expression for Ripple factor and Efficiency for Full Wave Rectifier. b) Compare FWR and Bridge rectifier.	6M 4M	3	2
8	a) The reverse leakage current of the transistor when in CB configuration is $0.3\mu A$ while it is $16\mu A$ when the same transistor is connected in CE configuration. Determine $\alpha$ , $\beta$ and $\gamma$ . b) Discuss the base width modulation.	6M 4M	4	3
	OR			
9	a) Explain input and output characteristics of transistor in CC configuration with neat diagram. b) The common base DC current gain of a transistor is 0.967. If the emitter current is 10 mA, what is the value of base current and collector current.	6M 4M	4	2
10	Illustrate the construction and principle of operation of JFET with necessary diagrams.	10M	5	3
	OR			
11	Describe the construction and working principle of Enhancement mode and depletion mode MOSFET and draw its characteristics.	10M	5	2