



**B. Tech II Semester Supplementary Examinations, January 2026**

**SEMICONDUCTOR DEVICES AND CIRCUITS**

*(Common to EEE, CSE, IT, CSE(AI&ML) & CSE(DS))*

**Maximum Marks: 70**

Date: 22.01.2026

Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

**Part-A**

All the following questions carry equal marks		(10X2M=20 Marks)	Marks	CO	BTL
1	What is doping.		2M	1	L1
2	Define static and dynamic forward resistances.		2M	1	L1
3	Write about Avalanche break down mechanism.		2M	2	L1
4	Draw V-I characteristics of SCR.		2M	2	L1
5	Define PIV and Ripple factor of a rectifier.		2M	3	L1
6	Draw the circuit of Bridge rectifier with capacitor filter.		2M	3	L1
7	Explain Thermal runaway.		2M	4	L1
8	Define Early effect.		2M	4	L1
9	Write the differences between BJT and FET.		2M	5	L1
10	Draw the symbols of JFET and MOSFET?		2M	5	L1

**Part-B**

Answer All the following questions.		(5X10M=50Marks)	Marks	CO	BTL
11	a) Explain how depletion layer is formed in P-N junction Diode with neat diagrams. b) Determine the value of forward current for a PN junction with $I_o = 15\mu A$ , $V_f = 0,6V$ , at $T=300K$ . Assume silicon diode.		6M 4M	1	L2
OR					
12	Explain the operation of a Tunnel Diode using Energy band diagrams.		10M	1	L2
13	Explain the V-I characteristics of Zener diode with neat sketches and write its applications..		10M	2	L2
OR					
14	a) Explain the operation of NPN Transistor. b) The emitter current in transistor is 4 mA. If the leakage current $I_{cbo}$ is 6milli amps and $\alpha$ is 0.98, find the collector and base currents.		5M 5M	2	L2
15	Draw the circuit and explain the operation of a Bridge Rectifier. Derive		10M	3	L2

	its RMS current and Ripple factor.			
	OR			
16	Draw and explain the circuit diagram and operation of full wave rectifier with $\pi$ section filter.	10M	3	L2
17	Explain the input and output characteristics of CE configured transistor circuit with a neat circuit diagram.	10M	4	L2
	OR			
18	Explain the Voltage divider biasing technique of a Transistor and derive its stability factor	10M	4	L2
19	With the help of neat circuit diagram explain the operation of N-channel JFET .	10M	5	L2
	OR			
20	Explain the construction and operation of a Depletion MOSFET and draw its characteristics.	10M	5	L2