



R22 Regulation

Subject code:4E2AP

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech II Semester Supplementary Examinations, January 2026
BASIC ELECTRICAL ENGINEERING
 (Common to CSE & CSE(AI&ML))

Maximum Marks: 60

Date: 22.01.2026

Duration: 3 hours

- Note: 1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

| All the following questions carry equal marks (10X1M=10 Marks) | | Marks | CO | BTL |
|----------------------------------------------------------------|--------------------------------------------------------|-------|----|-----|
| 1.a | What are Passive Elements? | 1M | 1 | L1 |
| b | State the Superposition theorem? | 1M | 2 | L1 |
| c | Define form factor of a sine wave | 1M | 1 | L1 |
| d | Define frequency | 1M | 1 | L1 |
| e | Explain why the transformer rating will be in KVA? | 1M | 3 | L4 |
| f | Define Efficiency of a transformer? | 1M | 3 | L1 |
| g | Why single-phase induction motor is not self-starting? | 1M | 3 | L4 |
| h | What is the function of DC motor. | 1M | 3 | L1 |
| i | What is MCCB? | 1M | 4 | L1 |
| j | List the Types of Batteries? | 1M | 4 | L1 |

Part-B

| Answer All the following questions. (5X10M=50Marks) | | Marks | CO | BTL |
|-----------------------------------------------------|-----------------------------------------------------------------|-------|----|-----|
| 2 | a) Explain about active elements with examples. | 5M | 1 | L2 |
| | b) Find the resistance between points A and B. | 5M | 1 | L3 |
| | | | | |
| OR | | | | |
| 3 | a) Explain the different types of sources with their symbols. | 5M | 1 | L2 |
| | b) State and explain Thevenin's theorem with an example. | 5M | 2 | L2 |
| 4 | a) Derive the equation for RMS value of voltage of a sine wave. | 5M | 1 | L2 |

| | | | | |
|----|---------------------------------------------------------------------------------------------------------------------------------------|----|---|----|
| | b) An alternating voltage is given by $V=230\sin314t$. Calculate: i) frequency ii) maximum value iii) average value iv) RMS value | 5M | 1 | L3 |
| | OR | | | |
| 5 | a) Derive an expression for the current in RC Series circuit with sinusoidal input. | 5M | 1 | L3 |
| | b) Derive the relation between phase and line values in a balanced Delta connected three phase system. | 5M | 1 | L3 |
| 6 | a) Explain the construction details of a transformer | 5M | 3 | L2 |
| | b) Explain the working principle of Auto transformer. | 5M | 3 | L2 |
| | OR | | | |
| 7 | a) Draw and explain equivalent circuit of a transformer | 5M | 3 | L3 |
| | b) Explain SC test on single phase transformer? | 5M | 3 | L2 |
| 8 | a) Derive the EMF equation of a dc generator | 5M | 3 | L3 |
| | b) Explain the torque slip characteristics of three phase induction motor. | 5M | 3 | L2 |
| | OR | | | |
| 9 | a) Explain the Principle of operation of DC Generator. | 5M | 3 | L2 |
| | b) Explain constructional details of three phase induction motor. | 5M | 3 | L2 |
| 10 | a) Explain the concept of earthing. | 5M | 4 | L2 |
| | b) Differentiate between ELCB and MCCB. | 5M | 4 | L3 |
| | OR | | | |
| 11 | a) Explain the concept of wiring systems. | 5M | 4 | L2 |
| | b) Compare between Meter board and Distribution board. | 5M | 4 | L3 |