



R20 Regulation *Subject code: 3E6BC*
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
(Autonomous, Accredited by NAAC with 'A' Grade)

B.Tech VI Semester Regular Examinations, June/July 2023

LINE-COMMUTATED AND ACTIVE RECTIFIERS
(Electrical and Electronics Engineering)

Maximum Marks: 70

Date:03.07.2023 Duration: 3 hours

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 What is the importance of freewheeling diode?
- 2 What are the factors that affect the output ripple of the capacitor-filter rectifier?
- 3 What do you understand by continuous current operation of thyristor converter?
- 4 Define the term voltage ripple factor and current ripple factor.
- 5 What are the advantages of using 12-pulse converter?
- 6 What is the reason of commutation overlap?
- 7 What are the advantages of using an isolated flyback converter?
- 8 What is the main difference between non-isolated DC-DC boost converters and single-switch AC-DC boost converters?
- 9 Give the advantages of a three-phase inverter over a single-phase inverter.
- 10 List the applications of a bidirectional boost converter.

Part-B

Answer All the following questions.

(10MX 5=50Marks)

- 11 A. In an aerospace application, a single-phase full-wave uncontrolled rectifier is supplied at 115 V, 400 Hz with source reactance of 0.15Ω . Assuming continuous ripple free load current of 5 A, compute the average load power. (5M)
B. What is the effect of commutation overlap? How to avoid this? (5M)

OR


- 12 Draw and explain the working principle of 3-phase diode rectifier with C filter. (10M)

- 13 A single phase fully controlled bridge converter operates in the continuous conduction mode from a 230 V, 50 Hz single phase supply with a firing angle $\alpha = 30^\circ$. The load resistance and inductances are 10Ω and 50 mH respectively. Find out the 6th harmonic load current as a percentage of the average load current. (10M)

OR

- 14 Draw the schematic and voltage waveform of a 3-phase thyristor rectifier with LC filter. (10M)

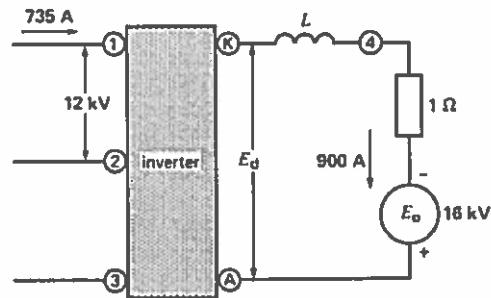- 15 A 16 kV dc source having an internal resistance of 1Ω supplies 900 A to a 12 kV, 3-phase, 6-pulse, 60 Hz inverter (see figure) (10M)



Calculate the following

- The dc current carried by each SCR.
- The dc voltage generated by the inverter.
- The required firing angle α .
- The effective value of the ac line currents.
- The reactive power absorbed by the inverter.

OR

- Describe with neat circuit diagram and associated waveforms, operation of 12-pulse converters. (10M)
- Explain the operation and working principle of a single-phase AC-DC single-switch boost converter. (10M)

OR

- Discuss the concept of isolation in power converters. (4M)
 - Explain the operation and working principle of an isolated single-phase AC-DC flyback converter. (6M)
- Describe the control structure and working principle of a three-phase inverter used in motor drive applications. (7M)
 - List the merits of isolated bidirectional AC-DC converter. (3M)

OR

- Explain the control structure of a bidirectional closed-loop converter and discuss their advantages in terms of power flow control. (10M)