



R20 Regulation *Subject code:3P5BA*
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
(Autonomous, Accredited by NAAC with 'A' Grade)
B.Tech V Semester Supplementary Examinations, June/July 2023

POWER ELECTRONICS
(Electrical and Electronics Engineering)

Maximum Marks: 70

Date:23.06.2023 Duration: 3 hours

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 List any two advantages of IGBT.
- 2 IGBT is a voltage-controlled device. Why?
- 3 What is meant by distortion factor?
- 4 Define Commutation.
- 5 What is the duty cycle in ON-OFF control method?
- 6 What is meant by DC chopper?
- 7 What is a series inverter?
- 8 Define space vector modulation.
- 9 Compare CSI and VSI.
- 10 What are the applications of a CSI?

Part-B

Answer All the following questions.

(10MX 5=50Marks)

- 11 Explain the steady state and switching characteristics of MOSFET. (10 Marks)
OR
- 12 Describe with circuit IGBT static I-V, transfer and turn-on and turn-off characteristics. (10 Marks)
- 13
 - A. What is the importance of snubber circuits in respect of Thyristors? (2 Marks)
 - B. Explain the operation of Single-Phase half-controlled bridge rectifier with R-Load with neat Sketch. (8 Marks)
OR
- 14
 - A. List the applications of Phase Controlled Rectifier. (3 Marks)
 - B. A three phase half wave thyristor rectifier delivers constant load current of 20A over the firing angle range of 0° to 60° . At these two firing angles, compute the power delivered to load for an AC input voltage of 300V from a delta star transformer? (7 Marks)
- 15 Describe the operation of single-phase full wave AC voltage controller with the help of voltage and current waveform. Also derive the expression for average value of output voltage. (10 Marks)
OR
- 16 Describe the working principle of boost converter with necessary circuit and waveforms. (10 Marks)
- 17
 - A. Differentiate the Current Source and Voltage Source Inverter. (5 Marks)
 - B. List the advantages, disadvantages, and applications of voltage source inverter. (5 Marks)

OR

- 18 Discuss the types of harmonic control for single phase inverter. (10 Marks)
- 19 Explain the principle of operation of 3-phase auto sequentially commutated CSI with power circuit. Draw the equivalent circuits and relevant waveforms. (10 Marks)
- OR
- 20 Explain the principle of operation of 3 phase voltage source inverter with 180° conduction mode with necessary waveforms and circuits. Also obtain the expression for line to line voltage. (10 Marks)