



Regulation R18

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code:2P4BB

B.Tech IV Semester Supplementary Examinations, July 2022

DIGITAL LOGIC DESIGN

(Electrical And Electronics Engineering)

Maximum Marks: 70

Date:22.07.2022 Duration: 3 Hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 What is Gray code?
- 2 How do you obtain dual of an expression?
- 3 What are don't cares?
- 4 What is minterm? Give example.
- 5 Compare combinational and sequential circuits.
- 6 Explain about binary cell.
- 7 What are the basic types of shift registers?
- 8 Differentiate PLA and PAL.
- 9 Define finite state machine.
- 10 Explain concept of minimal cover table.

Part-B

Answer All the following questions.

(5X10M=50Marks)

- 11 a) Convert the gray number 101101 into decimal, hex, octal [5+5]
b) Perform the subtraction in BCD using 9's complement method for 592.6-887.9
OR
- 12 Expand $(A+D')(A+C')(A'+B)(A'+B+C)$ into max terms and min terms. [10]
- 13 Minimize the following expression using K-map and realize using NAND Gates.
 $F(A,B,C,D) = \sum m(0,1,2,9,11) + d(8,10,14,15)$ [10]
OR
- 14 Explain about Multiplexer. Design a 32X1 multiplexer using 4x1 multiplexer. [10]
- 15 Draw the circuit diagram of J-K flip flop with NAND gates and explain its operation with the help of truth table. How race around condition is eliminated. [10]
OR
- 16 a) Explain about serial in parallel out shift register with a neat diagram.
b) Design a synchronous counter with T-flip flops that goes through the binary repeated sequence 0,1,3,7,6,4,0,1..... [5+5]
- 17 Design a mod-12 Ripple counter using T flip flops and explain its operation. [10]
OR
- 18 a) Explain different types ROMs.
b) Implement the following Boolean functions using PLA with 3 AND gates. [5+5]
 $F1(ABC) = \sum(3,5,7), F2 = \sum(4,5,7)$.
- 19 Explain about sequential circuits, state table and state diagram. [10]
OR
- 20 Explain about Mealy machine with circuit diagram. [10]