



Regulation R18

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code:2P3DC

B.Tech III Semester Supplementary Examinations, July 2022

ANALOG ELECTRONIC CIRCUIT ANALYSIS

(Electronics and Communication Engineering)

Maximum Marks: 70

Date:23.07.2022

Duration: 3 Hours

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 State Miller's theorem.
- 2 What is Gain of an amplifier?
- 3 Define Input Impedance.
- 4 Define f_T .
- 5 Define the gain bandwidth product of common Emitter amplifier.
- 6 Give any two comparisons of performance with BJT & JFET Amplifiers.
- 7 Define Negative feedback.
- 8 Define an Oscillator.
- 9 List the classification of power amplifiers.
- 10 Write down the applications of Tuned circuit?

Part-B

Answer all the questions

(10MX 5=50Marks)

- 11 Draw the circuit diagram of a CC amplifier along with its equivalent circuit. Derive expressions for A_v, R_i, A_i and R_o . (10M)
OR
- 12 Explain the Darlington Pair and derive the values of A_i, R_i, A_v & R_o . (10M)
- 13 Obtain an expression for CE short circuit current gain. (10M)
OR
- 14 Explain the Analysis of CD JFET Amplifier. (10M)
- 15 Derive the expression for the input resistance with feedback R_{if} and output resistance with feedback R_{of} in the case of (a) Voltage series feedback amplifier. (b) Voltage shunt feedback amplifier. (10M)
OR
- 16 Explain the different types of Feedback and the advantages of negative feedback. (10M)
- 17 Draw the circuit and Derive the expression for the frequency of oscillations of Colpitts oscillator circuit.(10M)
OR
- 18a. Explain the classification of Oscillators (5M)
- 18b Explain the operation of Oscillatory Circuit. (5M)
- 19 Draw the circuit and explain the working principle of a Class B power amplifier (10M)
OR
- 20 Explain single tuned Amplifier and list the advantages of tuned circuit. (10M)