



B.Tech III Semester Supplementary Examinations, July 2022
BASIC ELECTRICAL ENGINEERING
(MECHANICAL ENGINEERING)

Maximum Marks: 70

Date: 21.07.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- | | | |
|----|---|-----|
| 1 | Define node and branch. | 2 M |
| 2 | State Reciprocity theorem. | 2 M |
| 3 | Define instantaneous value | 2 M |
| 4 | Discuss the concept of phase and phase difference | 2 M |
| 5 | Define voltage regulation of a transformer | 2 M |
| 6 | Explain iron losses of the transformers | 2 M |
| 7 | State the function of commutator | 2 M |
| 8 | Define slip in induction motor | 2 M |
| 9 | What is the importance of Fuse | 2 M |
| 10 | What are the types of batteries | 2 M |


Part-B

Answer All the following questions.

(10M X 5=50Marks)

- 11 Find the current through 1Ω resistor using nodal analysis

10M

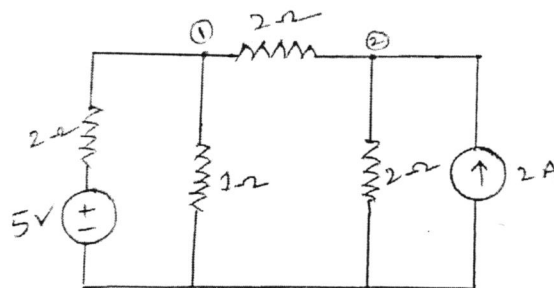


OR

- 12 a) State and explain Thevenin's theorem with suitable example.

5M

- b) Find Thevenin's equivalent circuit for the circuit shown below figure.

5M

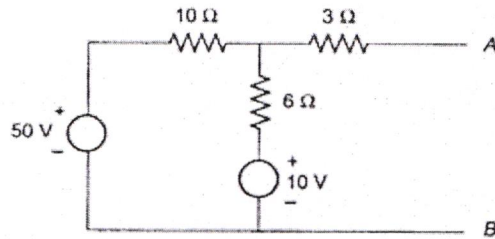

- 13 A voltage wave represented by $V=200\sin 314t$ find 10M
- i) Maximum value
 - ii) Average value
 - iii) RMS value
 - iv) Frequency
 - v) Time period
- OR
- 14 Derive the expression for impedance (Z), phase angle (Θ) and power factor ($\cos\phi$) for RLC series circuit with relevant phasors. 10M
- 15 a) Derive the Emf equation of transformer. 5M
 b) A 50KVA, 1100/400 V, 50Hz single phase transformer has 80 turns on the primary. Calculate 5M
- i) the number of turns on the secondary
 - ii) the full load primary and secondary currents and
 - iii) the maximum value of the flux
- OR
- 16 Explain the OC test of a single phase transformer with neat diagram 10M
- 17 a) Explain the constructional features of DC machine with neat diagram 5M
 b) Explain working principle of a DC motor? 5M
- OR
- 18 Explain the construction and working principle of 3-phase synchronous generator 10M
- 19 a) Explain briefly the concept of wiring system and earthing 5M
 b) Explain the types of wires and cables 5M
- OR
- 20 Explain about service mains, meter board and distribution board in detail. 10M