



**B.Tech III Semester Supplementary Examinations, July 2022**  
**ELECTRONIC CIRCUIT ANALYSIS**  
(ECE)

Maximum Marks: 70

Date:23.07.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 Discuss various possibilities of inter-stage coupling of amplifiers.
- 2 Draw a small signal low frequency model of a transistor.
- 3 Draw simplified high frequency model of CE amplifier.
- 4 Define the terms  $f_{\beta}$  and  $f_T$
- 5 Comparison of performance with BJT & JFET Amplifiers.
- 6 Draw the frequency response of CS amplifier with resistive load.
- 7 What is the effect of negative feedback on amplifier gain.
- 8 State the frequency for RC phase shift oscillator.
- 9 Write the advantages of class B push pull amplifier?
- 10 Write the classification of tuned amplifier?

Part-B

Answer All the following questions.

(10M X 5=50Marks)

- 11.a Draw the circuit diagram of a common base amplifier along with its equivalent circuit by using approximate analysis. Derive expressions for  $A_v$ ,  $R_i$ ,  $A_i$  and  $R_o$ . 7
  - b. What is non-linear distortion? List the causes for this type of distortion in amplifiers. 3
- OR
12. Draw the circuit for Cascode Amplifier. Explain its working, obtaining overall values of the circuit in terms of h-parameters. 10
- 13.a Obtain an expression for CE short circuit current gain. 6
  - b The CE short circuit current gain of transistor is 25 at a frequency of 2MHz, if  $f_{\beta}=200\text{kHz}$ . calculate (i)  $f_T$  (ii)  $h_{fe}$  (iii)  $|A_i|$  at a frequency of 10MHz. 4
- OR
- 14.a Give the typical values of various Hybrid- $\pi$  parameters 4
  - b Derive the expression of gain bandwidth product for current. 6

15. Explain the Analysis of CG JFET Amplifier 10  
OR
16. Draw the circuit diagram of common source amplifier with Diode connected load? 10  
Explain its operation.
- 17.a Discuss quantitatively about the effect of negative feedback on i) Gain ii) Bandwidth 5  
iii) Distortion
- 17.b Give the block diagram of a general feedback amplifier. State the function of each block 5  
OR
- 18.a Derive the expression for the frequency of Hartley oscillators 7
- b A Hartley oscillator is designed with  $L = 20\mu\text{H}$  and a variable capacitance. Find the 3  
Range of capacitance values if the frequency of oscillation is varied between 950 KHz  
to 2050 KHz.
- 19 Derive the expressions for maximum. Theoretical efficiency 'for 10  
(i) Transformer coupled  
(ii) Series fed amplifier what are their advantages and disadvantages.  
OR
- 20 Draw the circuit and explain the working principle of a complementary symmetry push- 10  
pull power amplifier and state its disadvantages?