

R20



~~Regulation 2018~~  
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY  
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 3P3DE

B.Tech III Semester Supplementary Examinations, July 2022  
**NETWORK ANALYSIS**

(ECE)

Maximum Marks: 70

Date: 29.07.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)


- 1 Define mutual induced e.m.f.
- 2 Explain the following terms  
(i) Tree (ii) Co- Tree
- 3 Define Transient response.
- 4 Define the term time constant.
- 5 Explain initial value theorem
- 6 Write the procedure for evaluating initial conditions
- 7 Define driving point function.
- 8 Define hybrid parameter.
- 9 What is the need of filter?
- 10 Write about the band rejection filter.

Part-B

Answer All the following questions.

(10M X 5=50Marks)

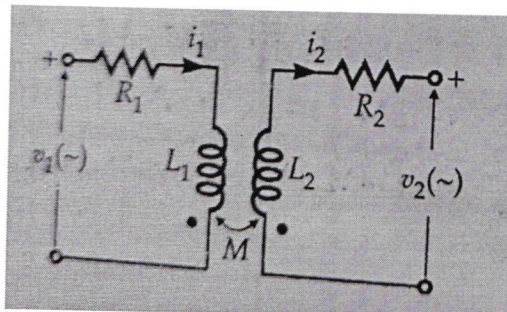
- 11 a) Explain about procedure for formation of a fundamental Tie- set matrix. 5  
b) Explain about formula for coefficient of coupling. 5  
OR
- 12 Fig represents a coupled coil circuit where  $L_1=20\text{mH}$ ,  $L_2=50\text{mH}$ . If the coefficient of mutual induction is 0.8, Find the Value of mutual induction and write down the mesh equations in time domain. 10



- 13 Derive the current expression for series RL circuit. 10

OR

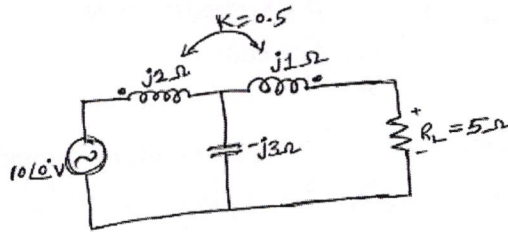- 14 Find the voltage drop across 5 ohm resistor 10



- 15 Write short notes on the following terms Laplace transformation and inverse Laplace transformation 10

OR

- 16 Write a short notes on convolution theorem, by using the convolution theorem, determine the inverse laplace transform of the following function  $H(s)=1/s^2(s+1)$ . 10

- 17 Determine z parameters in terms of y parameters. 10

OR

- 18 In the given network as shown in Fig. Find Z – parameters. 10

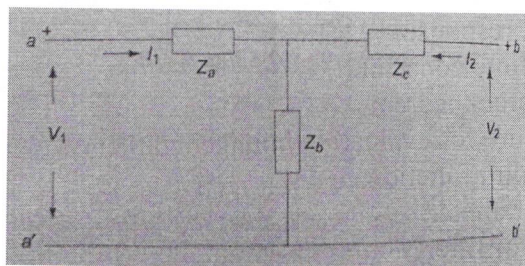


Fig. Network

- 19 Explain single tuned and double tuned filters. 10

OR

- 20 Explain design of m –derived low pass filter. 10